

ECE290 Fall 2012

Lecture 18

Dr. Zbigniew Kalbarczyk

Today


- Introduction to Control Unit
- Binary Multiplier Example
- Hardwire Control Unit for Binary Multiplier

Today

- Introduction to Control Unit
- Binary Multiplier Example
- Hardwire Control Unit for Binary Multiplier

Components of a Simple Computer

 - Focus on designing a **control unit** of a CPU in a simple computer



A Control Unit

- A **control unit** generates control input and control output signals that
 - activate micro-operations within data path to perform specified processing tasks
 - determine its own next state

Requirements on Control Units

- In **programmable** systems (use control memory and control program), a control unit consists of
 - Program counter (PC) and its decision logic
 - Logic to interpret instructions fetched from RAM or ROM
- In **non-programmable** systems (use gates + connections), a control unit determines
 - the operations to be performed and
 - the sequence of operations;
based on inputs and the status bits from data path.

Design Exercise: A Control Unit for Multiplication

- **Multiplication of Unsigned Numbers**

- If $0 < r < 2^n$ and $0 < s < 2^n$ then $2n$ bits suffice to hold the product of two n -bit binary number multiplication

- **Example:** Multiplicand **s=111**; Multiplier **r=110**

			1	1	1
		X	1	1	0
			0	0	0
		1	1	1	0
	1	1	1	0	0
1	0	1	0	1	0

Design Considerations

- Needed: **2n bit adder**
 - **Multiplicand**: register B of size= n
 - **Multiplier**: register Q of size= n
 - **Products**: register A of size= $2n$
- **Can we accomplish the same with n bit adder?**
- ***Design Idea:***
 - Repeatedly add s (multiplicand) to partial product
 - Keep shifting partial products to right so addition of s always occur in same place

Multiplication Execution with A, B and Q Registers

Init	Register A	=product		Register Q	=multiplier	
C	p2	p1	p0	r2	r1	r0
0	0	0	0	1	1	0

0 **0** **0** Add and then shift right

0	0	0	0	1	1	0
----------	----------	----------	----------	----------	----------	----------

C	p2	p1	p0	r2	r1	r0
0	0	0	0	0	1	1

1 **1** **1** Add and then shift right

0	1	1	1	0	1	1
----------	----------	----------	----------	----------	----------	----------

C	p2	p1	p0	r2	r1	r0
0	0	1	1	1	0	1

1 **1** **1** Add and then shift right


1	0	1	0	1	0	1
----------	----------	----------	----------	----------	----------	----------

C	p2	p1	p0	r2	r1	r0
0	1	0	1	0	1	0

Idea in Practice

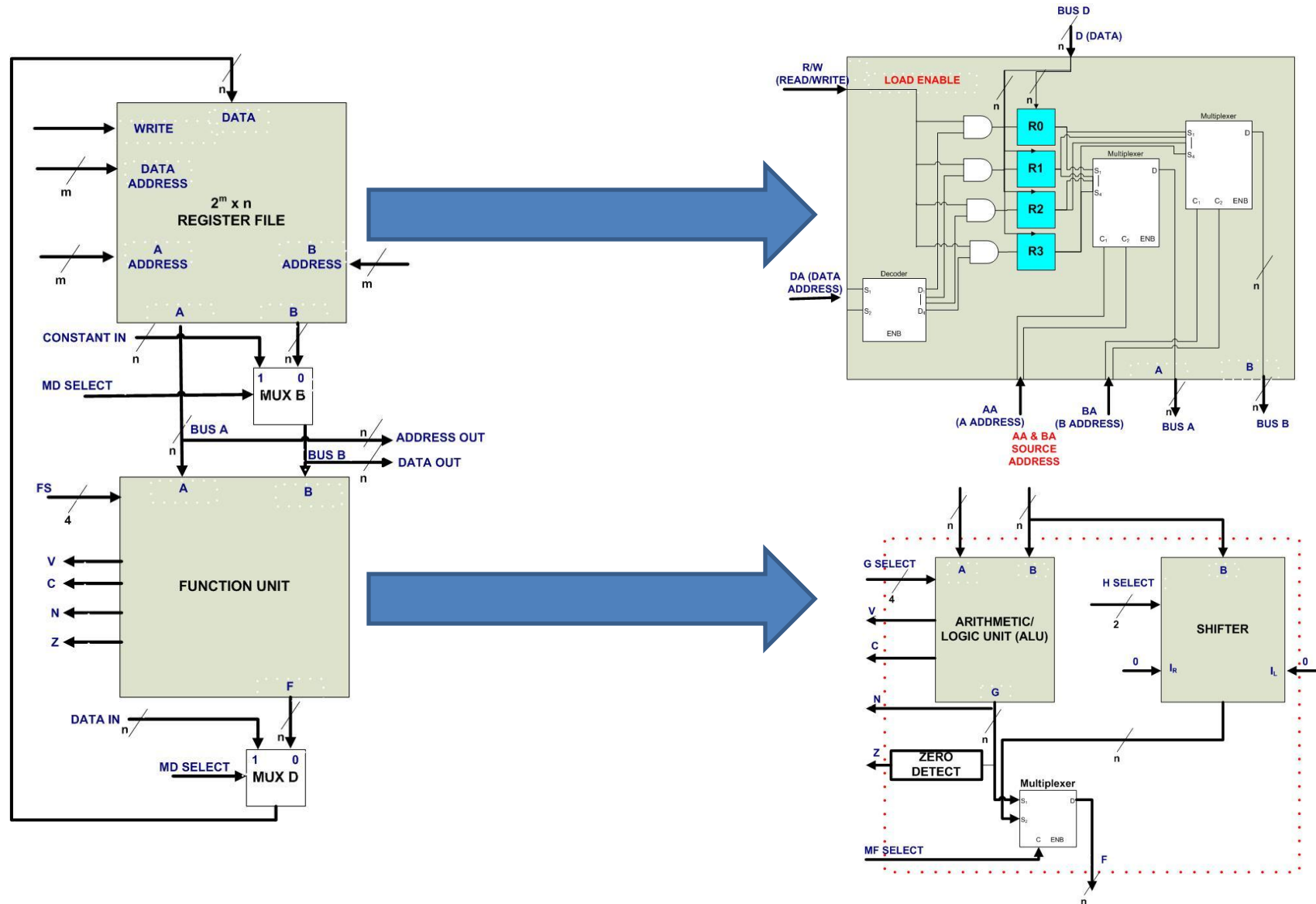
- 1. Load multiplier into Q register. As bits shift into Q from left, examine successive bits of multiplier at Q[0] (rightmost bit)
- 2. Set $C \leftarrow 0$ so that 0 shifts into leftmost bit of A register when no addition
- 3. Use counter P to count down from $n-1$ to 0
- 4. Define $Z=1$ when current value of P is 0...0

Data Path Components for Binary Multiplier



Binary Multiplier: Data Path

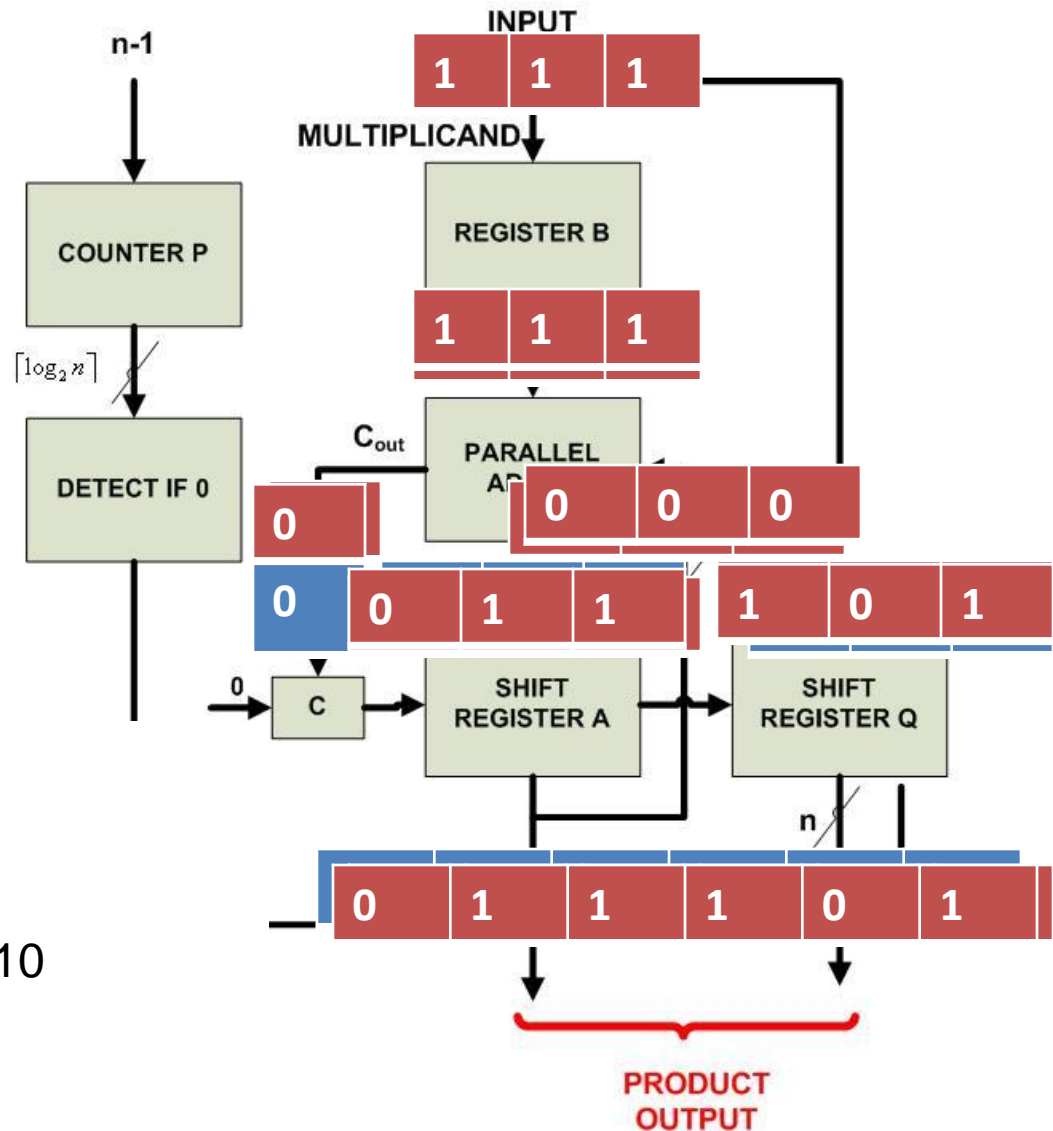- Block Diagram of Data Path Includes
 - Register File
 - Function Unit
 - Buses




Example: Step 1 of executing
111 x 110 ($n=3$)
Multiplicand=111; Multiplier = 110
Add and then shift right

Binary Multiplier: Data Path & Control Unit

- Block Diagram of Control Unit Includes

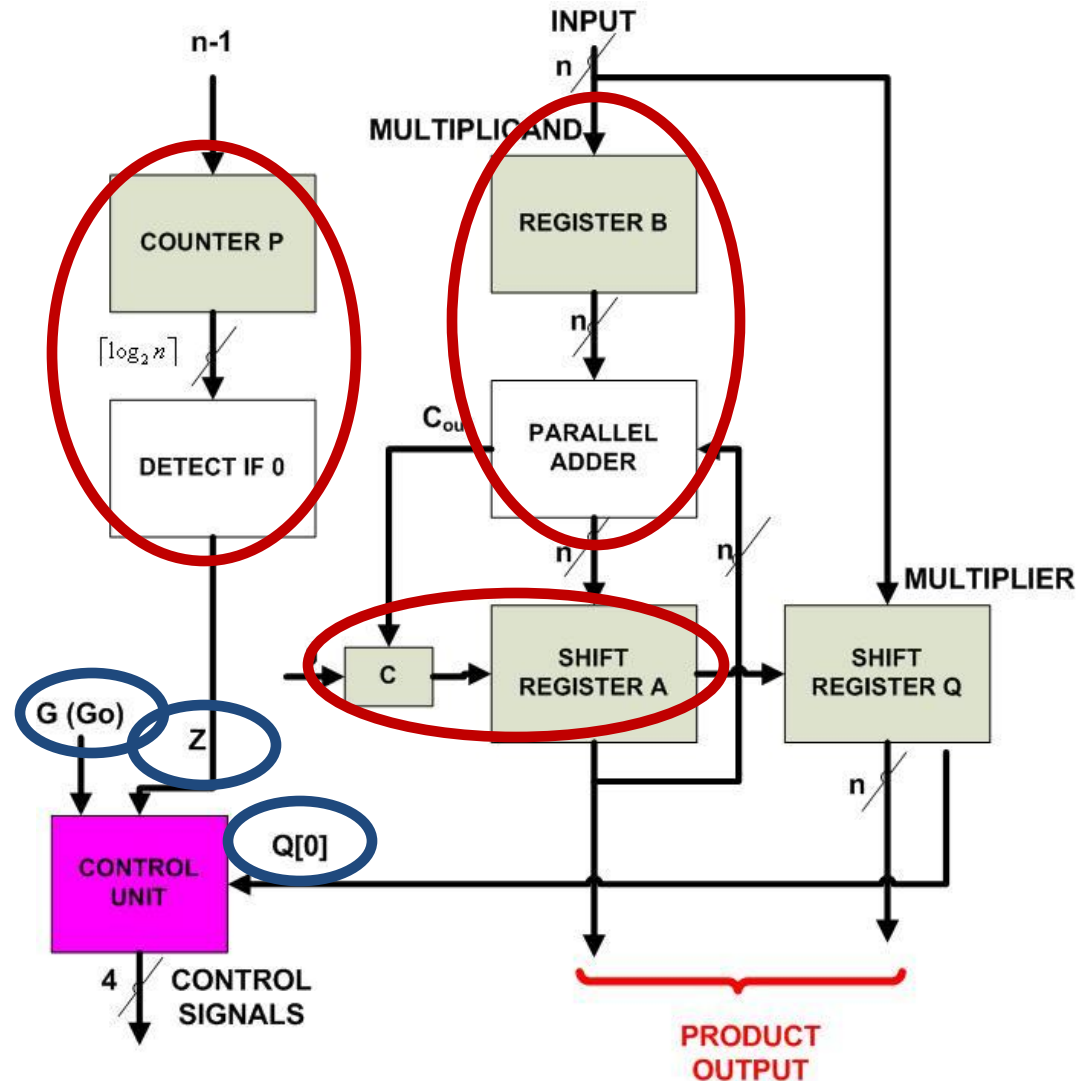- Status Bits ($Z = 1$ if $P=0$)
- Go signal ($Go=1$ to start multiplication)
- $Q[0]$
 - $Q[0]=1$ ~ add B register & updated A & C registers;
 - $Q[0]=0$ ~ A & C registers do not change




Algorithmic State Machines

- **Algorithmic State Machine (ASM) Chart**

- a sequence of events
- the **timing relationship** between the states
- Three basic elements
 - state box, decision box, conditional output box


- **State box**

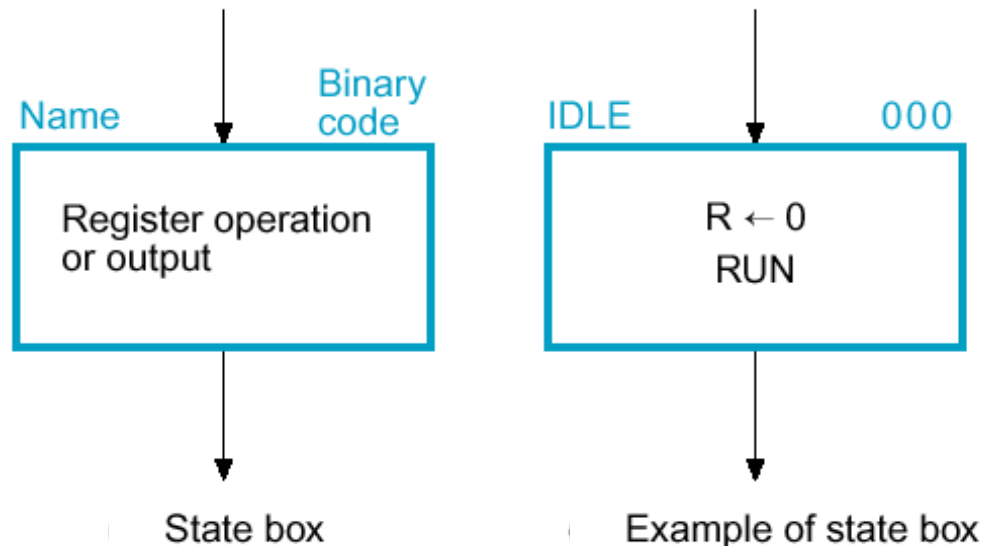

Algorithmic State Machines (2)

- **Decision box**

 
- Condition; single variable or Boolean expression




Decision box

Algorithmic State Machines (3)

- **Conditional output box**

 

Conditional output box

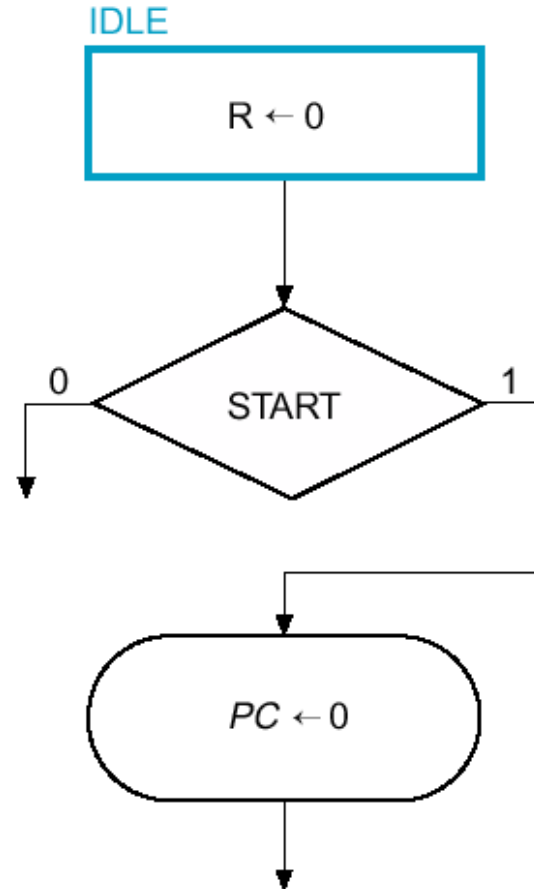


Example of decision and condition output box


Binary Multiplier Described by ASM Chart

- Assume:
 - Multiplicand is in register B and
 - Multiplier is in register Q
 - Loading of B and Q is not handled by the control unit explicitly
 - Result will be a concatenation of registers C, A and Q

ASM Chart for Binary Multiplier

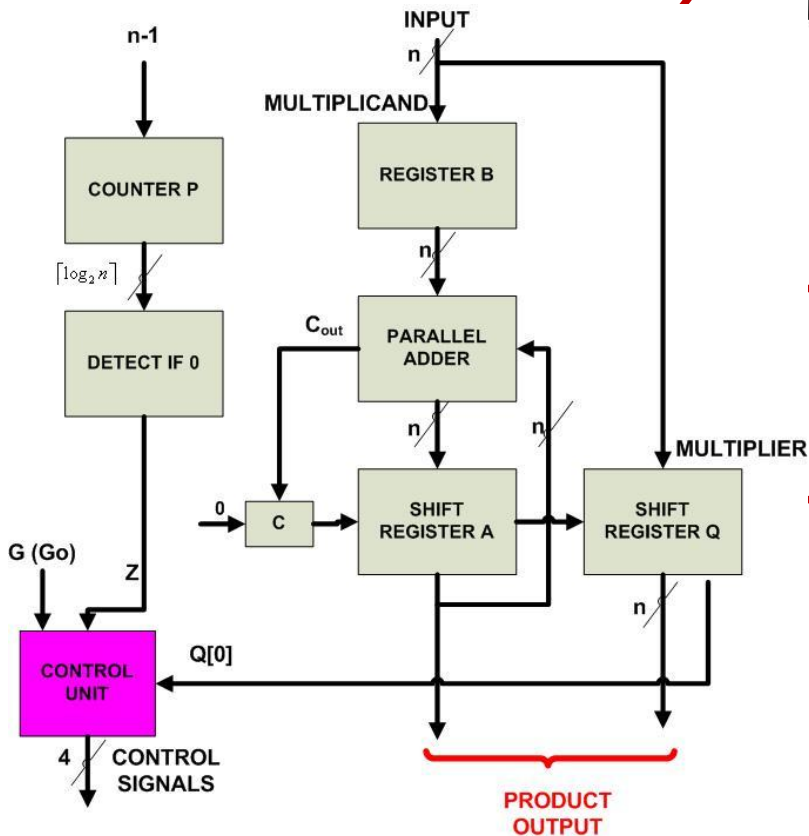

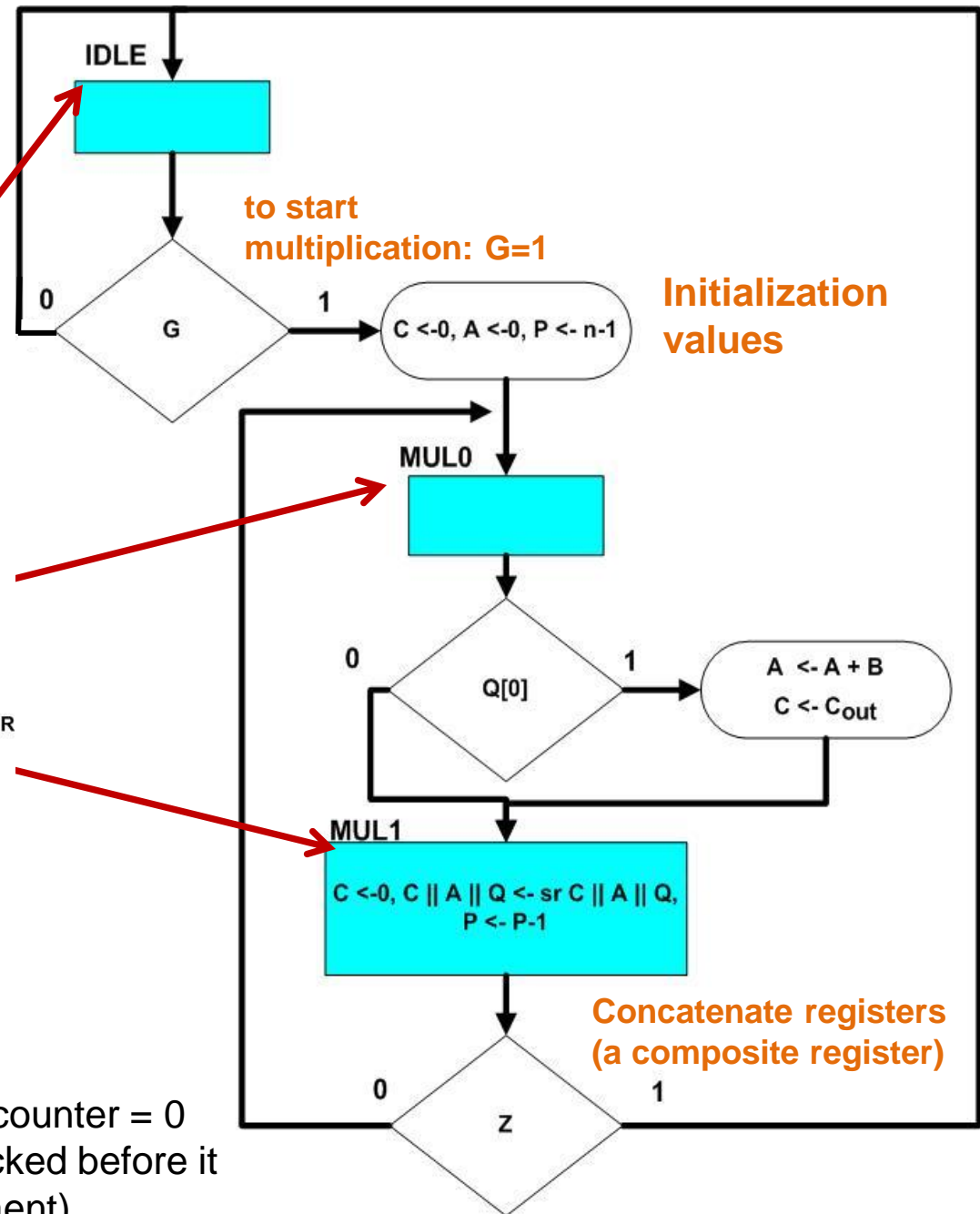$Z=1$ iff P counter = 0
(P is checked before it is decrement)



Hardwire Control Design


Two parts of the design:

- **Control of micro-operations**
 - Table of control signals defined in terms of states and inputs
- **Sequencing of the control unit and micro-operations**
 - Table of transition of states
- The logic for these two parts can be shared

Control of Micro-operations for Binary Multiplier


	Micro-operations	Control Signal Name	Boolean Expression
Register A	A \leftarrow 0	Initialize	IDLE * G
	A \leftarrow A + B	Load_AC	MUL0 * Q[0]
	Shift right (C A Q)	Shift_dec	MUL1
Register B	B \leftarrow IN	Load_B	LoadB
Register C	C \leftarrow 0	Clear_C	MUL1 + IDLE * G
	C \leftarrow C _{OUT}	Load_AC	----
Register Q	Q \leftarrow IN	Load_Q	LoadQ
	Shift right (C A Q)	Shift_dec	----
Register P	P \leftarrow n-1	Initialize	----
	P \leftarrow P - 1	Shift_dec	----

 Sequencing the Control Unit and Micro-operations



Sequencing Part of ASM Chart for the Binary Multiplier:

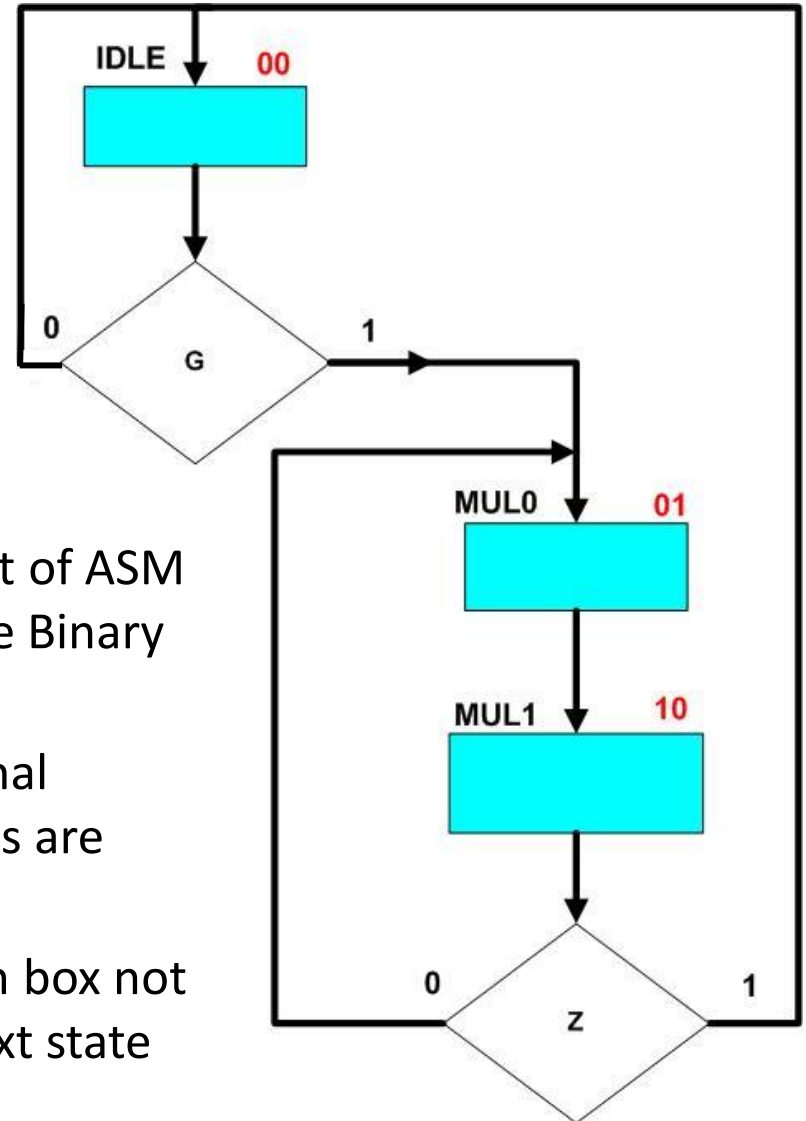- All conditional output boxes are removed
- Any decision box not affecting next state is removed



Hardwire Control: Implementation

1. Sequence register and decoder

- Use sequence register and decoder to generate a sequence of control signals from a control unit**


2. One flip-flop per state

- Use flip-flops in such a way that at any time only one flip-flop contains 1 and the rest contain 0

Hardwire Control: Sequence Register and Decoder Method


Method1: using sequence register and decoder:

1. Assign binary state to each ASM state
2. Keep binary state in sequence register
3. Use decoder to create a signal for each state
4. Design combinational logic to generate control signal and next state

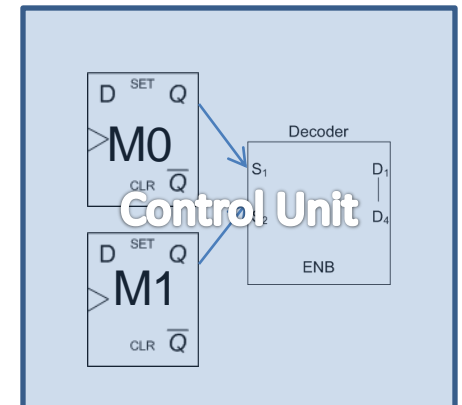






Method 1: From ASM to Control Signals

 - Starting Point:
 - Two inputs: G, Z (plus Q[0])
 - Three states: IDLE, MUL0, MUL1 (treated as Boolean variables)
- Needed:
 - 2 Flip-Flops for the sequence register
 - 2-to-4 line decoder (three states => only 3 out 4 decoder outputs will be used)
 - State Table



State Table for Sequence Register and Decoder

     - Derive relationships between inputs & current states to generate signals to get to next states



	Present States		Inputs		Next State		Decoder Outputs		
Name	M1	M0	G	Z	M1+	M0+	IDLE	MUL0	MUL1
IDLE	0	0	0	X	0	0	1	0	0
	0	0	1	X	0	1	1	0	0
MUL0	0	1	X	X	1	0	0	1	0
MUL1	1	0	X	0	0	1	0	0	1
	1	0	X	1	0	0	0	0	1
-----	1	1	X	X	X	X	X	X	X

IDLE=1 ~ I am not doing multiplication


Boolean Relationships

- Boolean Expressions for State Transitions


$$M0(t+1) = IDLE \cdot G + MUL1 \cdot \bar{Z}$$

$$M1(t+1) = MUL0$$

 - Boolean Expressions for Control Signals



Control Signal Name	Boolean Expression
Initialize	$IDLE * G$
Load_AC	$MUL0 * Q[0]$
Shift_dec	$MUL1$
Clear_C	$MUL1 + IDLE * G$
Load_B	$LoadB$
Load_Q	$LoadQ$

 

Method1: Control Unit for Binary Multiplier

