

# ECE290 Fall 2012

## Lecture 21

Dr. Zbigniew Kalbarczyk

# Today

- LC -3 Instruction Cycle
- LC-3 State Diagram
- Location of Control Signals in LC-3
- Values of Control Signals in LC-3 for ADD operation
- Values of Control Signals in LC-3 for NOT operation

# Instruction Cycle

## Phases of Instruction Cycle:

- **Fetch Phase:**
  - Fetch word from memory into instruction register (IR)
- **Decode Phase:**
  - Decode word in IR as instruction
- **Execute Phase**
  - Execute instruction


# Instruction Cycle: Fetch Phase

- **Fetch Phase:** fetch word from memory into IR
  - Place memory address in PC on the bus and load MAR with the memory address
  - Increment PC
  - Read from memory address specified in MAR to MDR
  - Copy MDR into IR

# Instruction

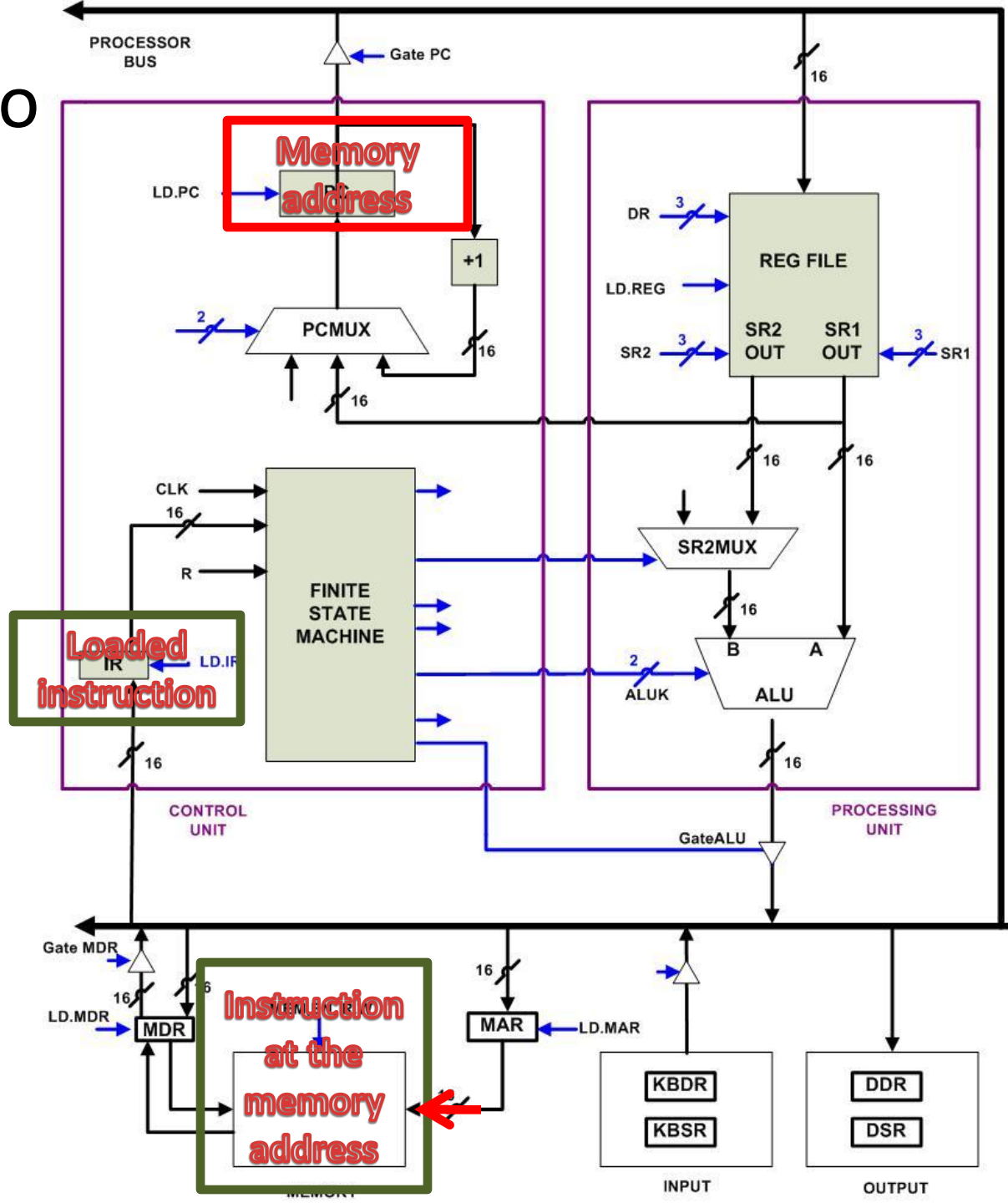
## Fetch Phase Operations:

- $MAR \leftarrow PC$ ,  
 $PC \leftarrow PC + 1$
- $MDR \leftarrow M[MAR]$   
(several clock cycles)
- $IR \leftarrow MDR$


 
# Instruction Cycle: Decode Phase

- **Decode Phase:** decode word in IR as instruction
  - Evaluate address
  - Fetch operands
  - Use opcode to determine next state of control unit
    - Example: ADD operation – next state is 1 (PC will be PC+1)




# Instruction Cycle: Execute Phase

- **Execute Phase:** execute instruction
  - Move data across data path to function unit
  - Activate function unit (includes Arithmetic/Logic Unit (ALU))
  - Set status bits (condition codes)
  - **Store results**
- **Example:**  $\text{ADD } \sim R4 \leftarrow R5 + R6$ 
  - Control signals to move R5, R6 to ALU
  - Control signals to compute addition
  - Set NZP
  - Control signals to move the result from ALU to R4
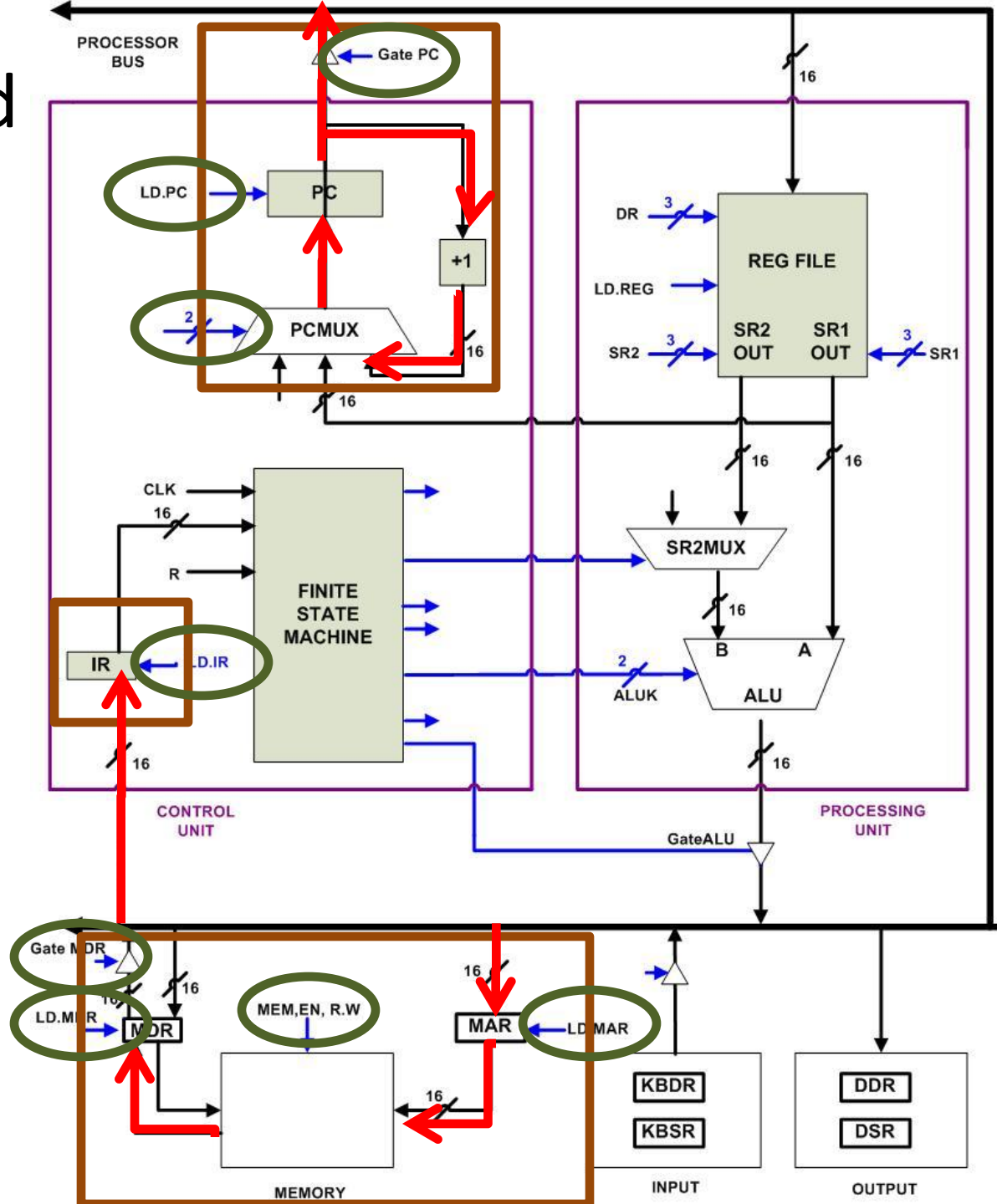
# Fetch Word


- **Wanted:** Move bits and words at the right time and to/from the right locations
- Fetch phase
  - Control signals?





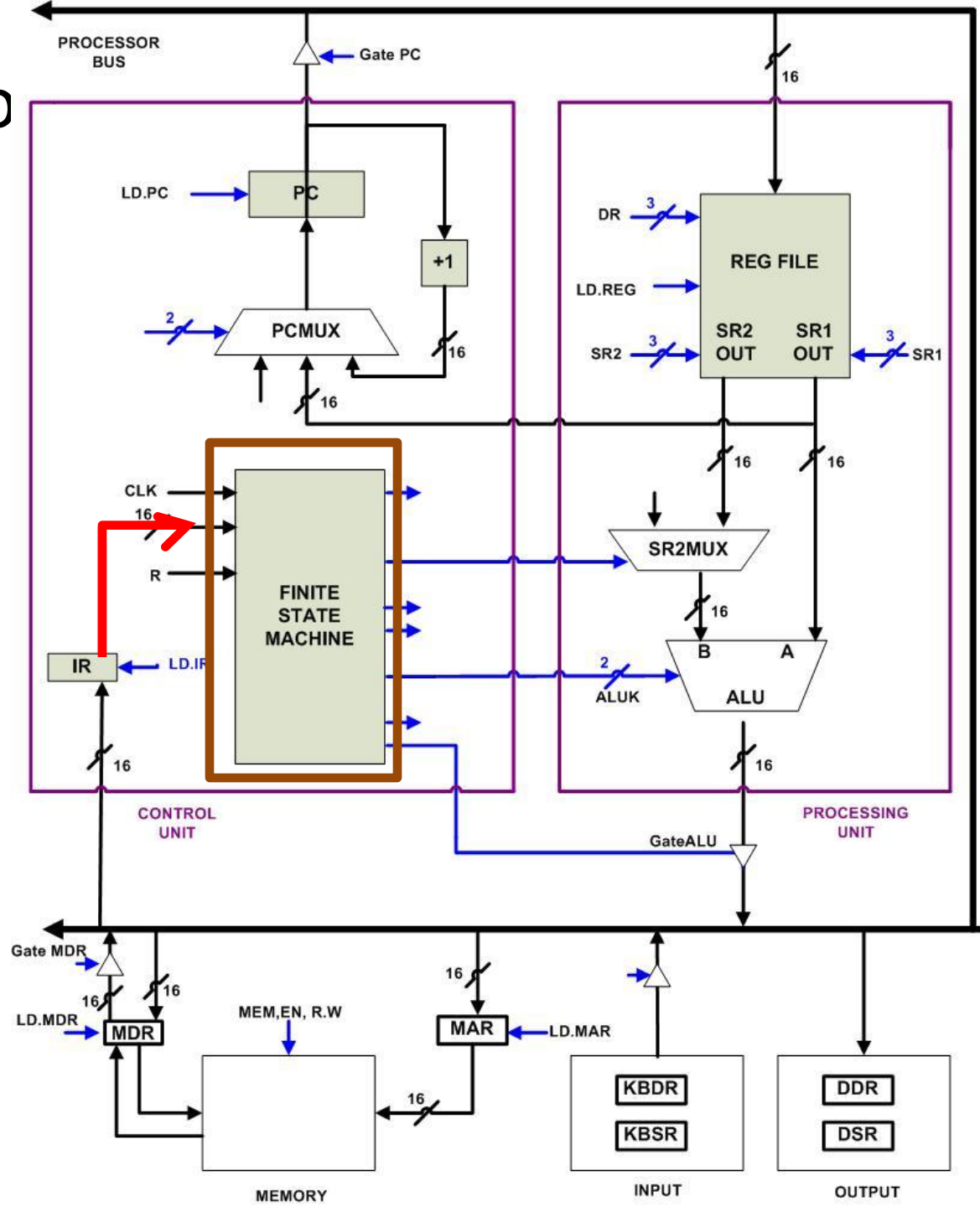
# Deco


- Decode phase
  - Control signals?
- Execute phase:
  - Control signals?



# Design of Finite State Machine

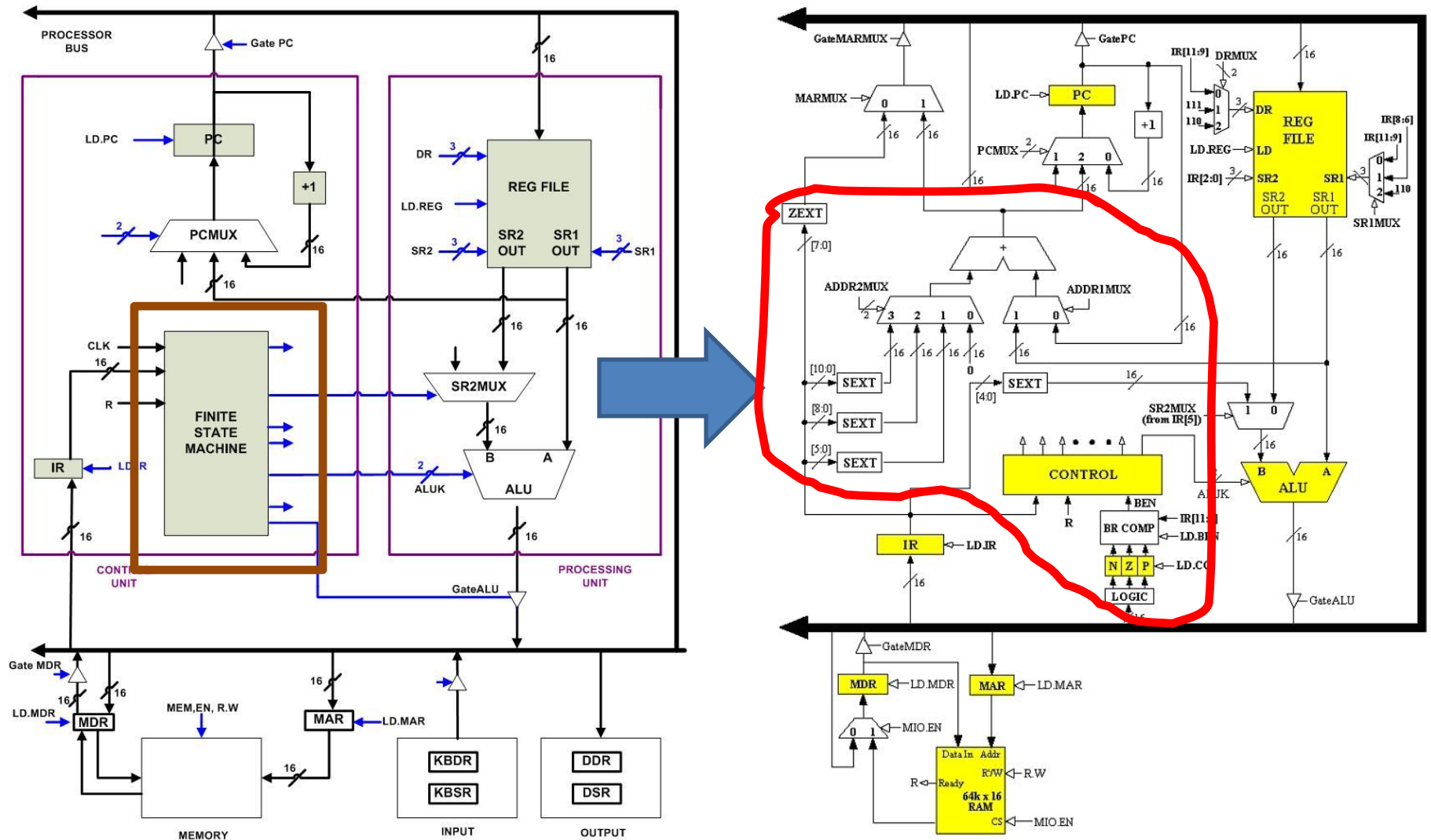

# LC-3: Abbreviated State Diagram

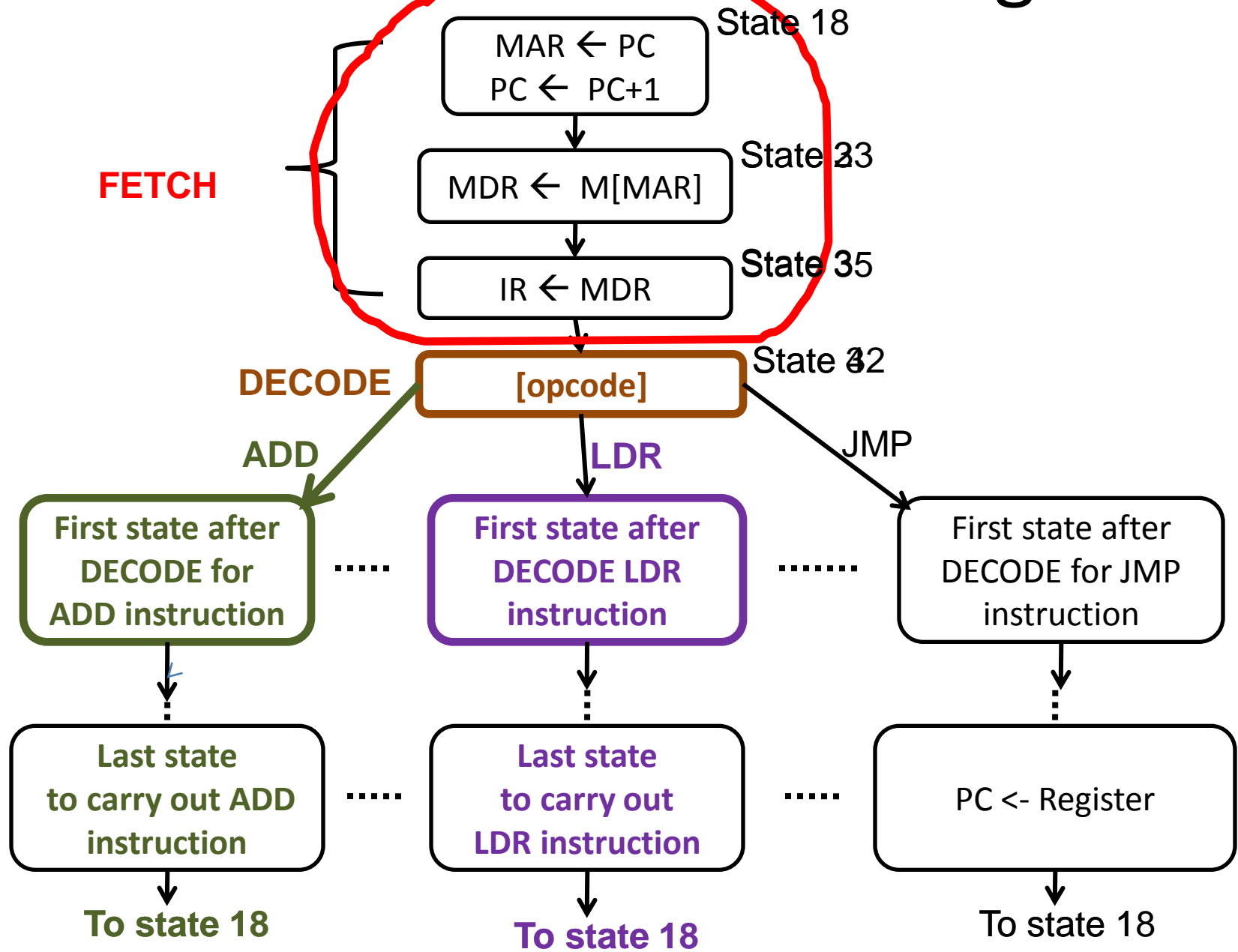

Where is the  
Wanted: deco

	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	
ADD <sup>+</sup>	0001				DR				SR1		0	00				SR2	DR ← SR1 + SR2; set NZP
ADD <sup>+</sup>	0001				DR				SR1		1				imm5		DR ← SR1 + SEXT(imm5); set NZP
AND <sup>+</sup>	0101				DR				SR1		0	00				SR2	DR ← SR1 AND SR2; set NZP
AND <sup>+</sup>	0101				DR				SR1		1				imm5		DR ← SR1 AND SEXT(imm5); set NZP
BR	0000				n	z	p										IF ((n·N)+(z·Z)+(p·P)) THEN PC ← PC + SEXT(PCoffset9)
JMP	1100				000				BaseR							000000	PC ← BaseR
JSR	0100				1											PCoffset11	R7 ← PC PC ← PC + SEXT(PCoffset11)
JSRR	0100				0	00			BaseR							000000	R7 ← PC PC ← BaseR
LD <sup>+</sup>	0010				DR											PCoffset9	DR ← M[PC + SEXT(PCoffset9)]; Set NZP
LDI <sup>+</sup>	1010				DR											PCoffset9	DR ← M[M[PC + SEXT(PCoffset9)]]; Set NZP
LDR <sup>+</sup>	0110				DR				BaseR							offset6	DR ← M[BaseR + SEXT(offset6)]; Set NZP
LEA <sup>+</sup>	1110				DR											PCoffset9	DR ← PC + SEXT(PCoffset9); Set NZP
NOT <sup>+</sup>	1001				DR				SR							111111	DR ← NOT(SR); Set NZP
RET	1100				000				111							000000	PC ← R7
ST	0011				SR											PCoffset9	M[PC + SEXT(PCoffset9)] ← SR
STI	1011				SR											PCoffset9	M[M[PC + SEXT(PCoffset9)]] ← SR
STR	0111				SR				BaseR							offset6	M[BaseR + SEXT(offset6)] ← SR

superscript "+" denotes instructions that update the condition bits NZP


# Decoding Operands

## Where is the operand?

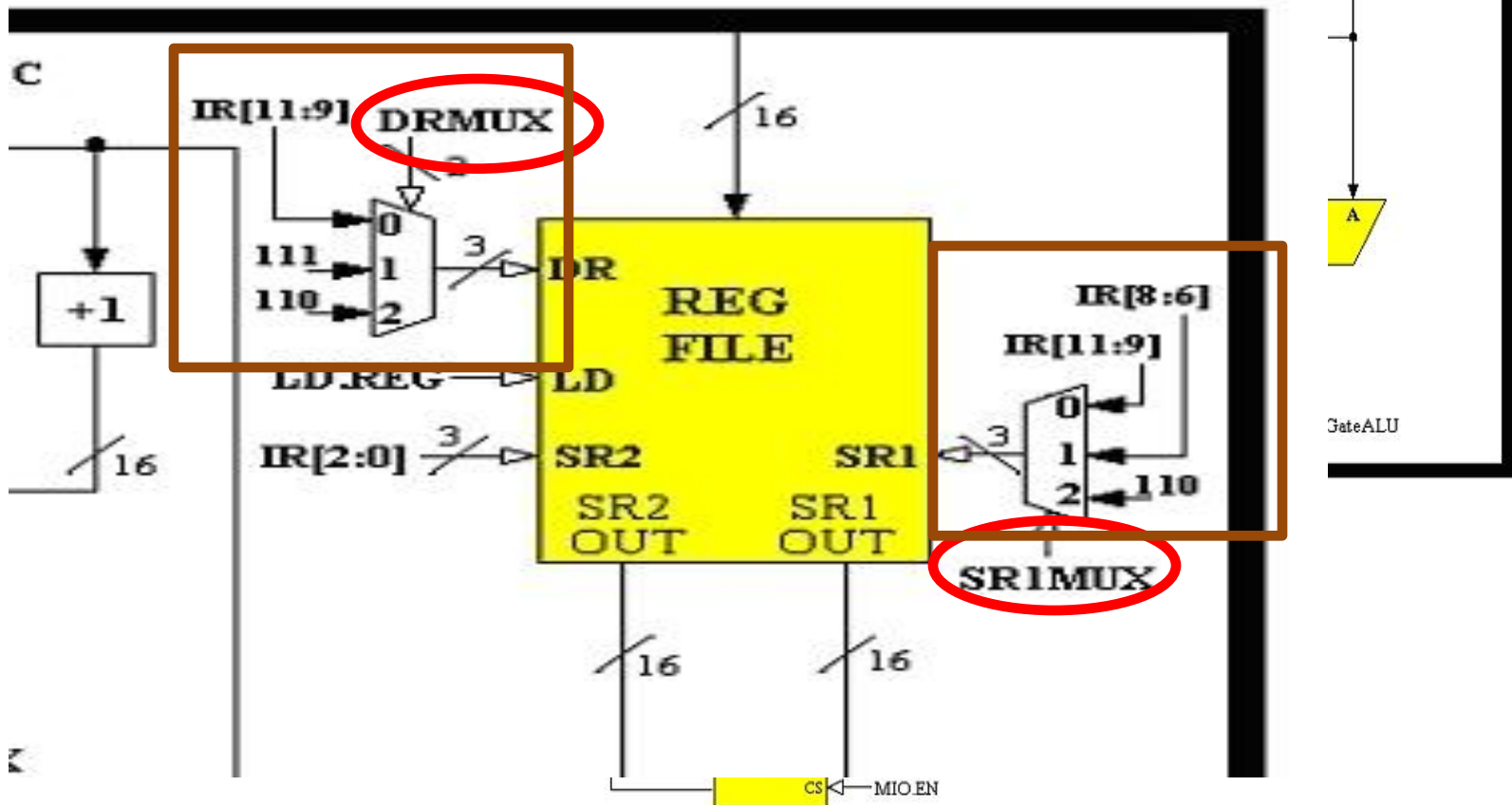
**Wanted: decode operand addresses and values**

- Direct Decode: SR2 input: IR[2:0]
- Need MUX:
  - SR1 input: IR[11:9] or IR[8:6] or 110
  - DR input: IR[11:9] or 111 or 110
- Note:
  - R6 (110) ~ stack pointer
  - R7 (111) ~ used for subroutine calls

- Where are the inputs in the architecture?




- Where are all **input** architecture?

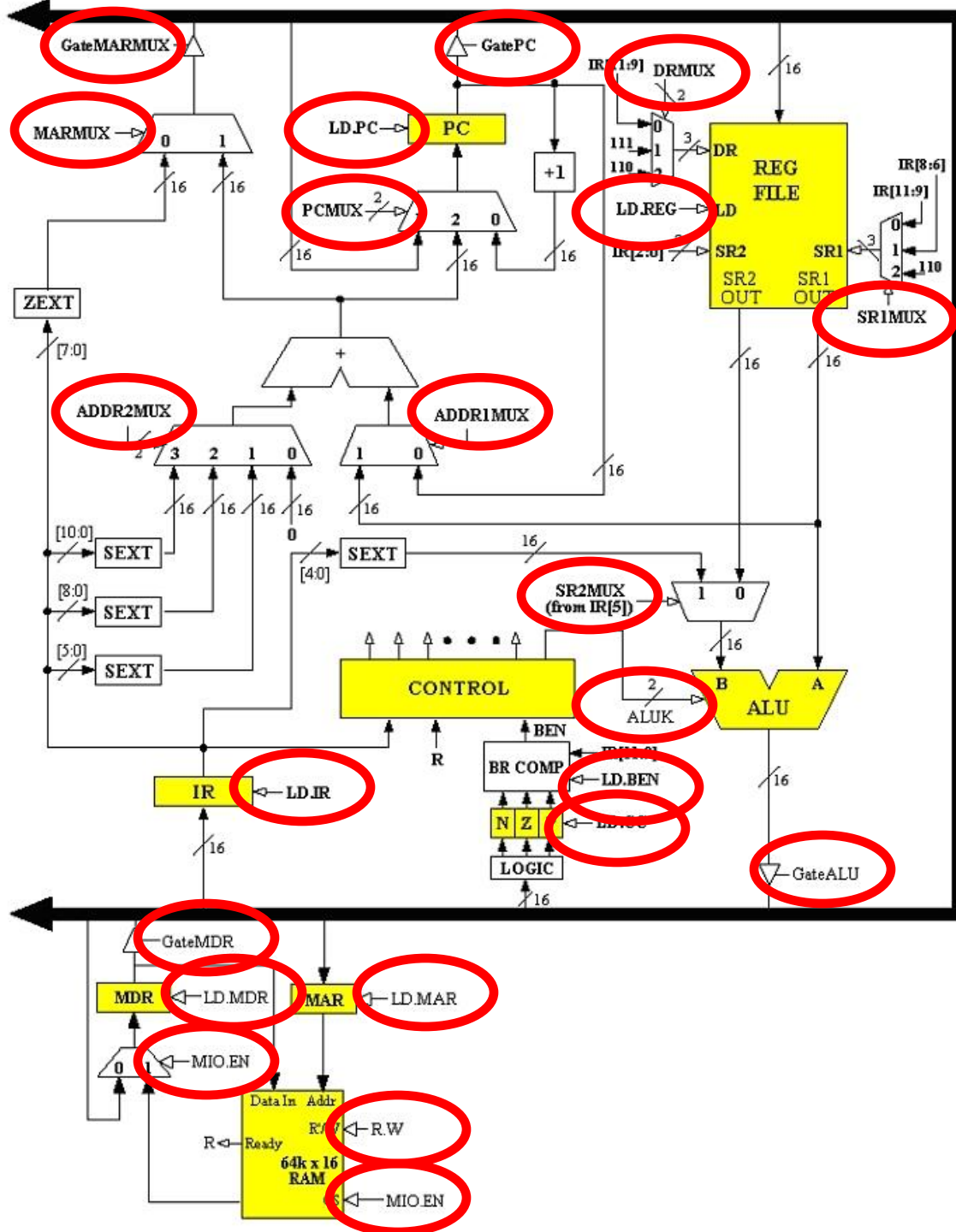


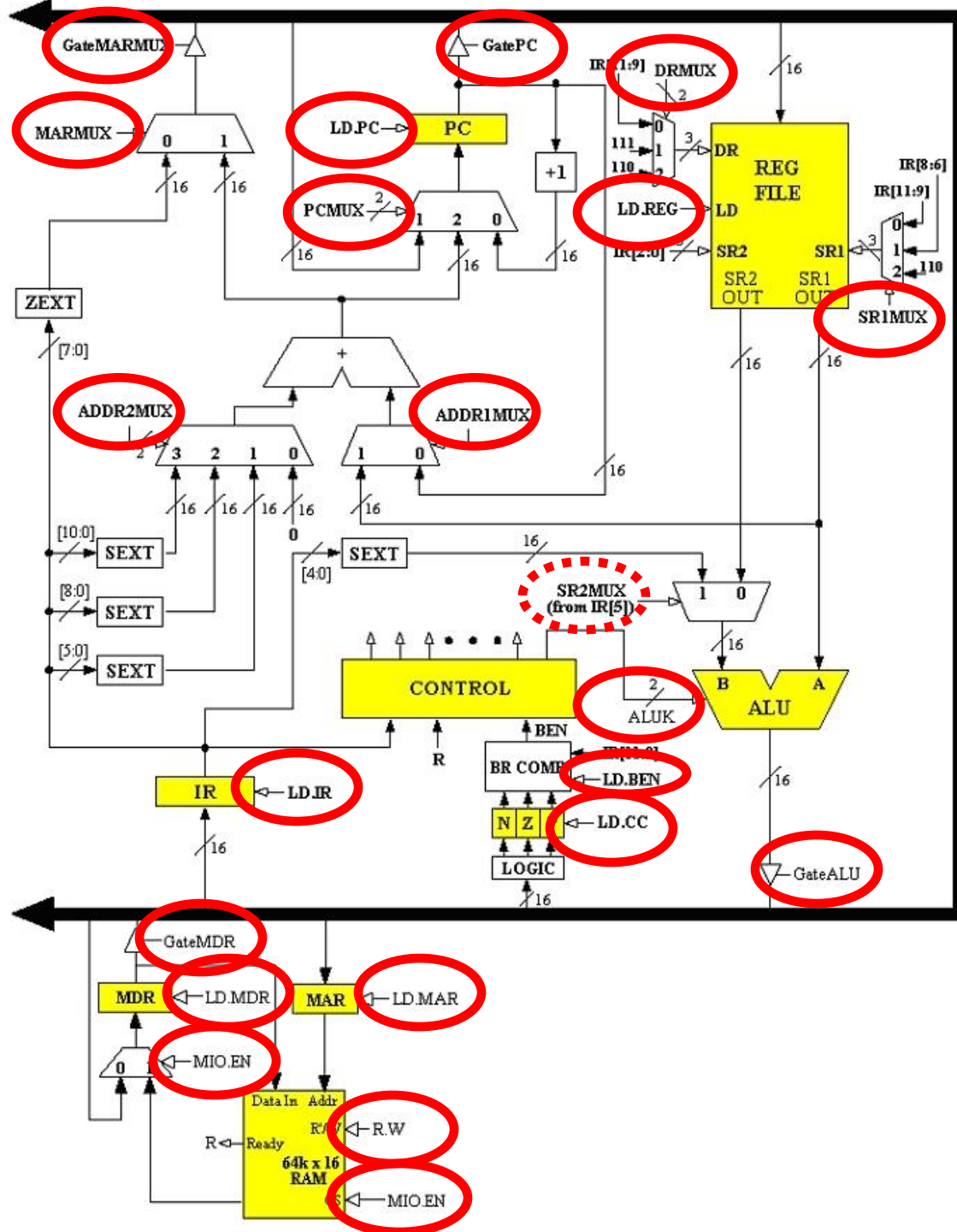
# Control Signals in

- Summary:
  - GateXX: 4
  - LD.XX: 7
  - xxMUX: 6 (+1 IR[5])
  - ALUK: 1
  - MIO.EN: 1
  - R.W: 1






# Control Signals in

Control Signal	Number of Signals	Total Number of Bits for Control Signals
GateXX	4	4
LD.XX	7	7
xxMUX	6	10
ALUK	1	2
MIO.EN	1	1
R.W	1	1

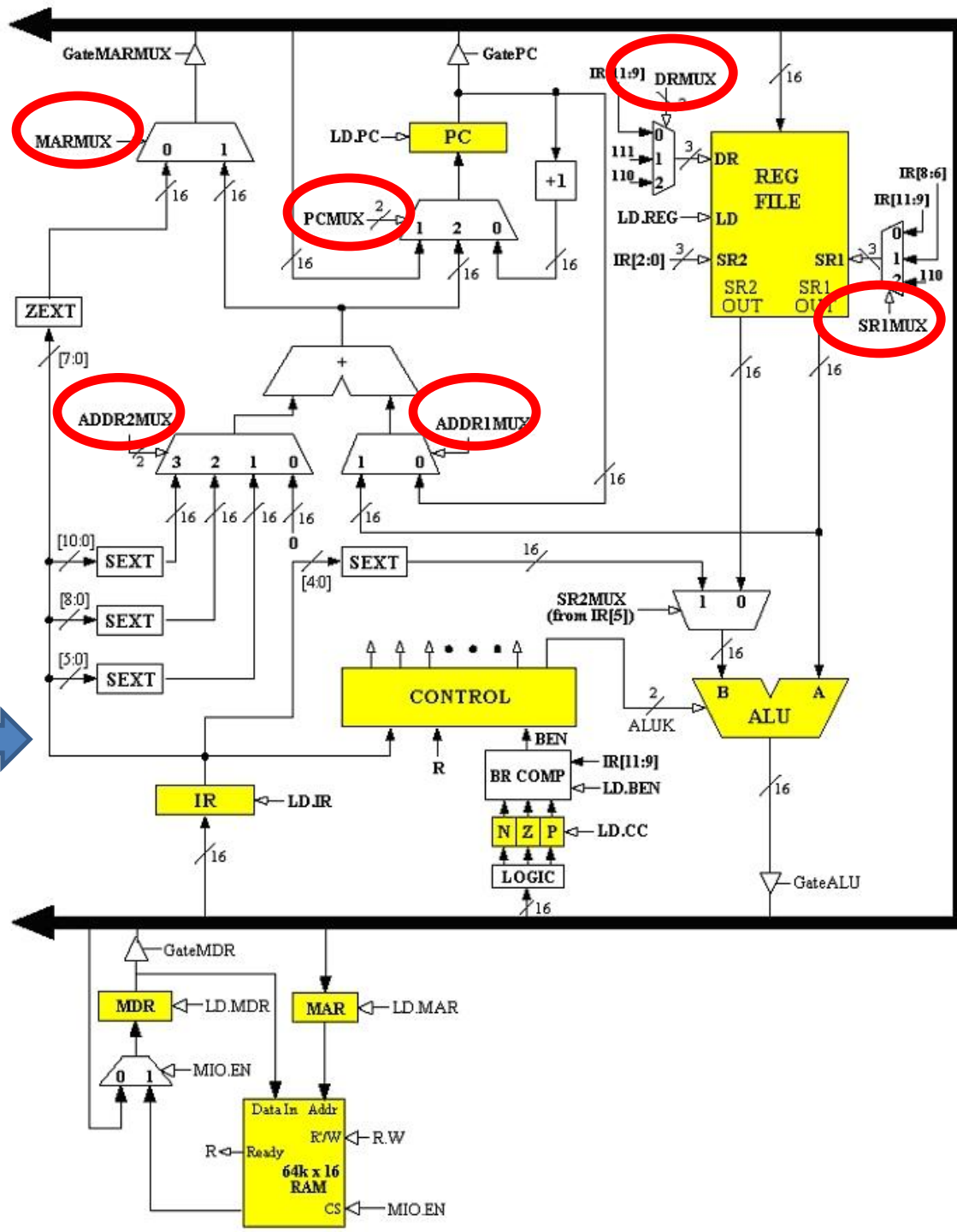**Generate: 25 bits of control signals!!!**



# Execute Phase: ADD Operation

- Task: execute ADD (1 microinstruction)
  - $SR1 (DR) \leftarrow SR1 + SR2$ , Load NZP
  - $SR1 (DR) \leftarrow SR1 + \#2$ , Load NZP



0	0	0	1	0	0	1	0	0	1	0	0	0	0	1	0
0	0	0	1	0	0	1	0	0	1	1	0	0	0	1	0

**What are the control signals needed for the execution of the microinstruction?**

# Execute Phase: ADD Operation – Bus Gate Signals

- Task:  $SR1 (DR) \leftarrow SR1 + SR2$ , Load NZP

- 0 0 0 1 0 0 1 0 0 1 0 0 0 0 1 0

## – GateXX:

- GatePC=0
- GateMARMUX = 0
- GateMDR = 0
- GateALU = 1

Control Signal	Number of Signals	Total Number of Bits for Control Signals
GateXX	4	4
LD.XX	7	7
xxMUX	6	10
ALUK	1	2
MIO.EN	1	1
RW	1	1

# Execute Phase: ADD Operation – Load signals

- Task:  $SR1 (DR) \leftarrow SR1 + SR2$ , Load NZP

- 0 0 0 1 0 0 1 0 0 1 0 0 0 0 1 0


– LD.XX:

- LD.PC=0
- LD.BEN = 0
- LD.MAR = 0
- LD.MDR = 0
- LD.IR=0
- LD.REG =1
- LD.CC = 1

Control Signal	Number of Signals	Total Number of Bits for Control Signals
GateXX	4	4
LD.XX	7	7
xxMUX	6	10
ALUK	1	2
MIO.EN	1	1
RW	1	1
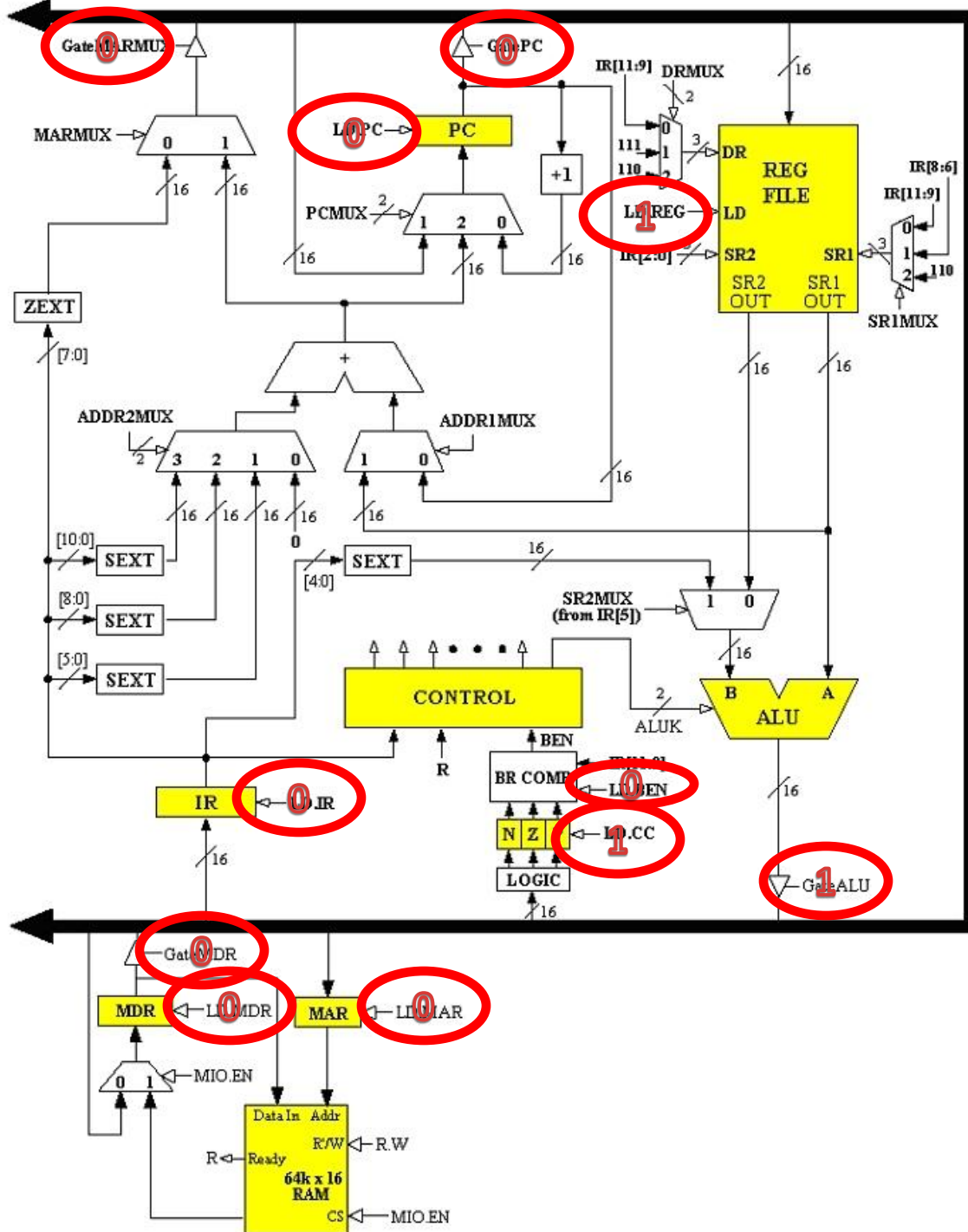
# Control Signals

- Current Assignment of Control Signals:
  - GateXX:
  - LD.XX:



# Execute Phase: ADD Operation – Multiplexer Selection Signals

- Task:  $SR1 (DR) \leftarrow SR1 + SR2$ , Load NZP

0 0 0 1 0 0 1 0 0 1 0 0 0 0 1 0



SR2MUX=IR[5] = 0

- Control signals:

– xxMUX:

- SR1MUX = 01 (IR[8:6])
- DRMUX = 00 (IR[11:9])
- MARMUX = x
- PCMUX = x
- ADDR1MUX = x
- ADDR2MUX = x

Control Signal	Number of Signals	Total Number of Bits for Control Signals
GateXX	4	4
LD.XX	7	7
xxMUX	6	10
ALUK	1	2
MIO.EN	1	1
RW	1	1

# Execute Phase: ADD Operation – Other Control Signals

- Task:  $SR1 (DR) \leftarrow SR1 + SR2$ , Load NZP

0	0	0	1	0	0	1	0	0	1	0	0	0	0	1	0
---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---


- Control signals:

- $ALUK = 00$
- $MIO.EN = 0$
- $RW = x$

Control Signal	Number of Signals	Total Number of Bits for Control Signals
GateXX	4	4
LD.XX	7	7
xxMUX	6	10
ALUK	1	2
MIO.EN	1	1
RW	1	1
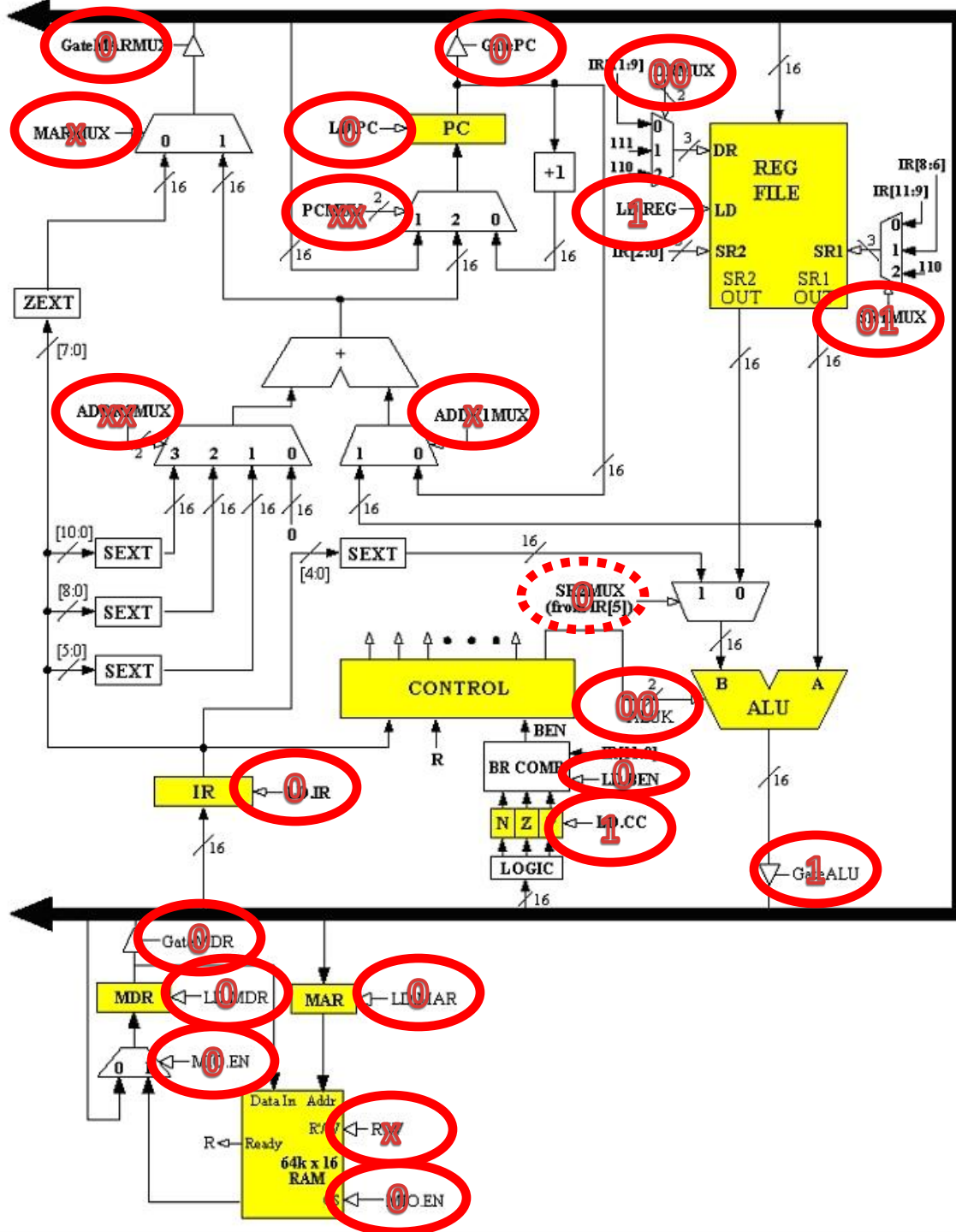
# Control Signals


- All Assignments of Control Signals:
  - GateXX:
  - LD.XX:
  - xxMUX:
  - ALUK:
  - MIO.EN:
  - R.W:




 
# Control Signals

- Selections based on control signals:
  - SR1 selected based on IR[8:6]
  - SR2 selected based on IR[2:0]
  - DR selected based on IR[11:9]
  - What to add selected based on IR[5]



# Execute Phase: ADD Operation – Summary of Control Signals

Signal Name	Binary Value
GateMAR MUX	0
GateMDR	0
GateALU	1
GatePC	0

Signal Name	Binary Value
ALUK	00
MIO.EN	0
R.W	X

Signal Name	Binary Value
LD.BEN	0
LD.MAR	0
LD.MDR	0
LD.IR	0
LD.PC	0
LD.REG	1
LD.CC	1


Signal Name	Binary Value
MARMUX	X
PCMUX	XX
ADDR1MUX	X
ADDR2MUX	XX
DRMUX	00
SR1MUX	01

# LC-3 Control Word Fields

- no Interrupt or Exception Control signals!


Signal Name	Binary Value	Signal Name	Binary Value	Signal Name	Binary Value
LD.BEN	0	GateMAR MUX	0	MARMUX	X
LD.MAR	0	GateMDR	0	PCMUX	XX
LD.MDR	0	GateALU	1	ADDR1MUX	X
LD.IR	0	GatePC	0	ADDR2MUX	X
LD.PC	0			DRMUX	0
LD.REG	1			SR1MUX	0
LD.CC	1				

Signal Name	Binary Value
ALUK	00
MIO.EN	0
R.W	X

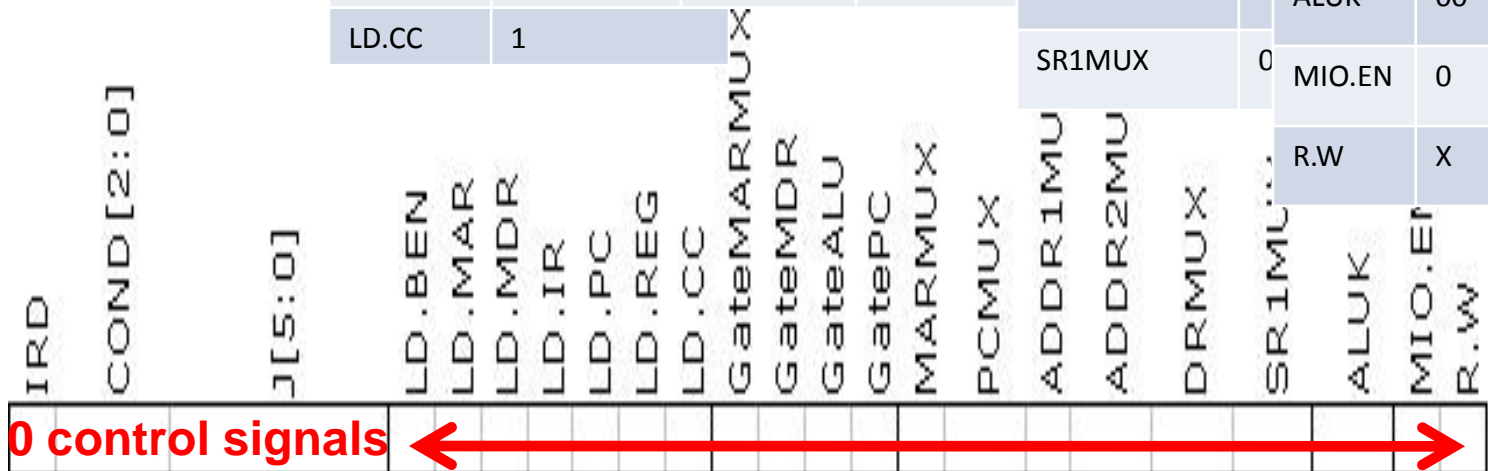

# Execute Phase: NOT Operation

 - Task:  $SR1(DR) \leftarrow NOT(SR1)$ , Load NZP



- Directly derived control signals:
  - SR2MUX=1 (IR[5])
  - SR1MUX = 01 (IR[8:6])
  - DRMUX = 00 (IR[11:9])

# Execute Phase: NOT Operation – Summary of Control Signals

- Control signals

Signal Name	Binary Value
GateMAR MUX	0
GateMDR	0
GateALU	1
GatePC	0

Signal Name	Binary Value
ALUK	10
MIO.EN	0
R.W	x

Signal Name	Binary Value
LD.BEN	0
LD.MAR	0
LD.MDR	0
LD.IR	0
LD.PC	0
LD.REG	1
LD.CC	1

Signal Name	Binary Value
MARMUX	X
PCMUX	XX
ADDR1MUX	X
ADDR2MUX	XX
DRMUX	00
SR1MUX	01

# Control Signals

- Selections based on control signals:
  - SR1 selected based on IR[8:6]
  - DR selected based on IR[11:9]
  - What to add selected based on IR[5]

