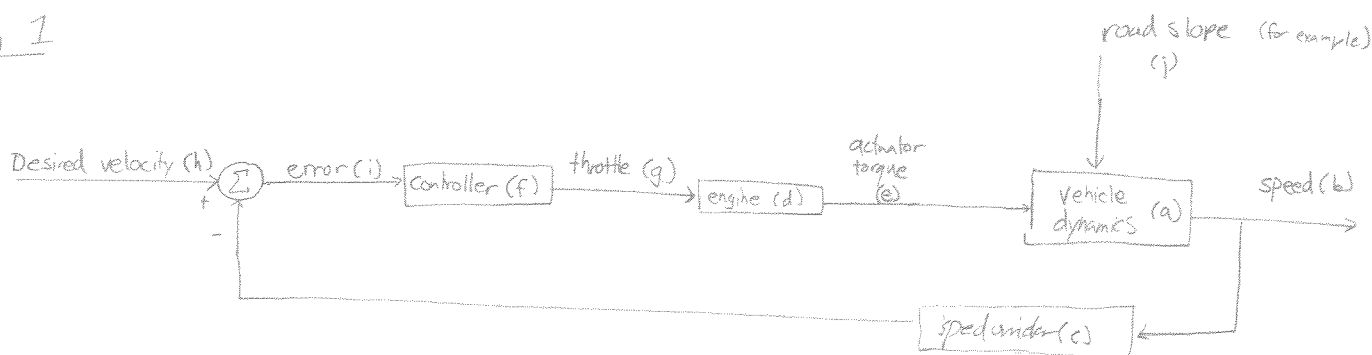


Homework 1 Solutions

Units

Problem 1



throttle: flow of fuel/air into engine

torque: twisting effort from the engine

(other disturbances: road slope, frictional losses, etc.)

speed sensor: velocity sensor

units:

desired velocity: m/s

error: m/s


throttle: kg/s

torque: Nm


slope: radians

speed: m/s

Problem 2

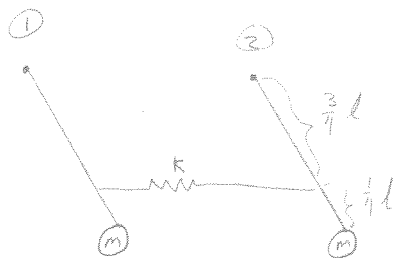

Draw free body diagrams

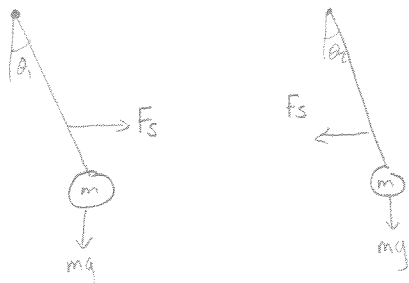

Sum the moments

$$\sum M_i = I_i \ddot{\theta}_i = -mg l \sin(\theta_i) + F_s \left(\frac{3}{4}l\right) \cos \theta_i$$

$$m l^2 \ddot{\theta}_1 = -mg l \sin(\theta_1) + k(\Delta x) \left(\frac{3}{4}l\right) \cos \theta_1$$

$$m l^2 \ddot{\theta}_2 = -mg l \sin(\theta_2) + k \left[\left(\frac{3}{4}l\right) (\sin \theta_2 - \sin \theta_1) \right] \left(\frac{3}{4}l\right) \cos \theta_2$$

use small angle approximation

$$\sin \theta \approx \theta \quad \cos \theta \approx 1$$

$$m l^2 \ddot{\theta}_1 = -mg l \theta_1 + \frac{9}{16} k l^2 (\theta_2 - \theta_1)$$

$$0 = m l \ddot{\theta}_1 + m g \theta_1 + \frac{9}{16} k l (\theta_1 - \theta_2)$$

or

$$0 = \ddot{\theta}_1 + \frac{g}{l} \theta_1 + \frac{9}{16} \frac{k}{m} (\theta_1 - \theta_2) = 0$$

Similarly for θ_2


$$\sum M_2 = m l^2 \ddot{\theta}_2 = -mg l \sin \theta_2 - F_s \left(\frac{3}{4} l \right) \cos \theta_2$$

$$m l^2 \ddot{\theta}_2 = -mg l \sin \theta_2 - k \left(\frac{3}{4} l \right) (\sin \theta_2 - \sin \theta_1) \left(\frac{3}{4} l \right) \cos \theta_1$$

$$m l^2 \ddot{\theta}_2 = -mg l \theta_2 - \frac{9}{16} k l^2 (\theta_2 - \theta_1)$$

$$\boxed{0 = m l \ddot{\theta}_2 + mg \theta_2 + \frac{9}{16} k l (\theta_2 - \theta_1)} \quad \text{or} \quad \boxed{0 = \ddot{\theta}_2 + \frac{g}{l} \theta_2 + \frac{9}{16} \frac{k}{m} (\theta_2 - \theta_1) = 0}$$

Problem 3

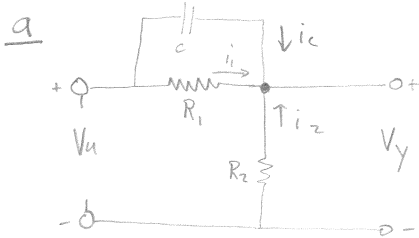

sum currents at node


$$i_1 + i_2 + i_c = 0$$

$$\frac{V_u - V_y}{R_1} + C \frac{d}{dt} (V_u - V_y) + \frac{(0 - V_y)}{R_2} = 0$$

$$\frac{V_u}{R_1} - \frac{V_y}{R_1} + C (\dot{V}_u - \dot{V}_y) - \frac{V_y}{R_2} = 0$$

$$\boxed{C \dot{V}_u + \frac{1}{R_1} V_u = C \dot{V}_y + \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_y}$$

X

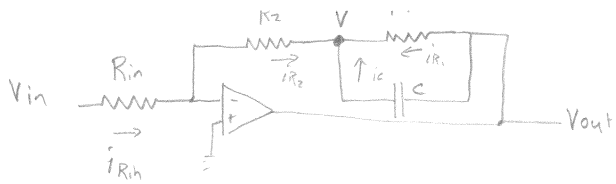

Sum currents at V

$$i_{R_2} + i_c + i_{R_1} = 0$$

$$(1) \quad \frac{V_{out} - V}{R_1} + \frac{(0 - V)}{R_2} + C(\dot{V}_{out} - \dot{V}) = 0$$

Sum currents going in to op amp

$$i_{R_{in}} = i_{R_2}$$

$$\frac{V_{in} - 0}{R_{in}} = \frac{0 - V}{R_2}$$


$$(2) \quad V = -\frac{R_2}{R_{in}} V_{in}$$

plug (2) into (1)

$$\frac{V_{out} + \frac{R_2}{R_{in}} V_{in}}{R_1} + \frac{\frac{R_2}{R_{in}} V_{in}}{R_2} + C(\dot{V}_{out} + \frac{R_2}{R_{in}} \dot{V}_{in}) = 0$$

$$\frac{V_{out}}{R_1} + \frac{R_2}{R_1 R_{in}} V_{in} + \frac{1}{R_{in}} V_{in} + C\dot{V}_{out} + C \frac{R_2}{R_{in}} \dot{V}_{in} = 0$$
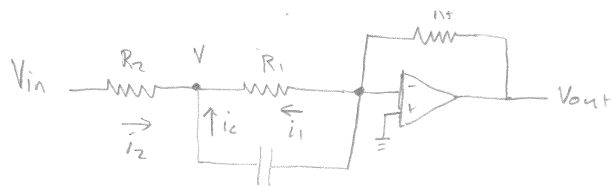
$$\boxed{\frac{R_2}{R_{in}} C \dot{V}_{in} + \frac{1}{R_{in}} \left(1 + \frac{R_2}{R_1}\right) V_{in} = -C \dot{V}_{out} - \frac{1}{R_1} V_{out}}$$



Sum at V

$$i_2 + i_c + i_1 = 0$$

$$\frac{V_{in} - V}{R_2} + C(0 - \dot{V}) + \frac{0 - V}{R_1} = 0$$

$$(1) \quad \frac{V_{in} - V}{R_2} - C\dot{V} - \frac{V}{R_1} = 0$$

all current flows through R_2 and R_f :

$$i_2 = i_{R_f}$$

$$\frac{V_{in} - V}{R_2} = \frac{0 - V_{out}}{R_f}$$

$$(2) \quad V_{in} + \frac{R_2}{R_f} V_{out} = V$$

plug (2) into (1)

$$\frac{V_{in} - (V_{in} + \frac{R_2}{R_f} V_{out})}{R_2} - C(\dot{V}_{in} + \frac{R_2}{R_f} \dot{V}_{out}) - \frac{(V_{in} + \frac{R_2}{R_f} V_{out})}{R_1} = 0$$


simplify

$$C\dot{V}_{in} + \frac{1}{R_1} V_{in} = \frac{-1}{R_f} \left[R_2 C \dot{V}_{out} + \left(1 + \frac{R_2}{R_1} \right) V_{out} \right]$$

4

assume $x=0$ when the plates are touching. Additionally, the free length of the spring is where $x=0$

a) draw a free body diagram of b

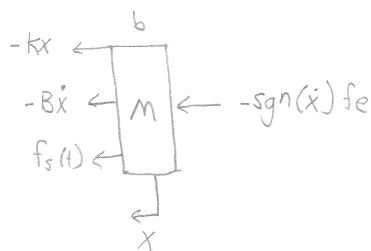

$\text{sgn}(\dot{x})$ returns the sign of $\dot{x}$ (-1 or 1). f_e is the electrical resisting force

$$\sum F_b = M\ddot{x} = -Kx - B\dot{x} + f_s(t) - f_e \text{sgn}(\dot{x})$$

$$M\ddot{x} + B\dot{x} + Kx + f_e \text{sgn}(\dot{x}) = f_s(t)$$

$$f_e = \frac{q^2}{2\epsilon A}$$

$$(1) \quad M\ddot{x} + B\dot{x} + Kx + \frac{q^2}{2\epsilon A} \text{sgn}(\dot{x}) = f_s(t)$$

draw electrical diagram



Kirchoff's voltage law

$$e = V - IR - L\dot{I}$$

$$I = \dot{q}$$

$$e = V - \dot{q}R - L\ddot{q}$$

e , the voltage on the plate is equivalent to

$$e = \frac{q}{C} = \frac{qx}{\epsilon A}$$


$$\frac{qx}{\epsilon A} = V - R\dot{q} - L\ddot{q}$$

$$M\ddot{x} + B\dot{x} + Kx + \frac{q^2}{2\epsilon A} \text{sgn}(\dot{x}) = f_s(t)$$

$$L\ddot{q} + R\dot{q} + \frac{x}{\epsilon A} q = V$$

b) no, the $\text{sgn}(\dot{x})$, q^2 , and qx terms prevent a useful linearized system

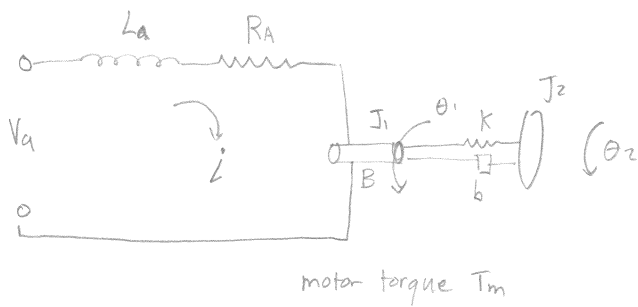c) As a microphone, the output is the current I , or equivalently $\dot{q}$



Rotor

$$\sum M = J_1 \ddot{\theta}_1 = T_m - k(\theta_1 - \theta_2) - b(\dot{\theta}_1 - \dot{\theta}_2) - B\dot{\theta}_1$$

$$J_1 \ddot{\theta}_1 = k_i i - k(\theta_1 - \theta_2) - b(\dot{\theta}_1 - \dot{\theta}_2) - B\dot{\theta}_1$$

Load

$$\sum M = J_2 \ddot{\theta}_2 = k(\theta_1 - \theta_2) + b(\dot{\theta}_1 - \dot{\theta}_2)$$

Circuit

Kirchoff's voltage l:

$$V_a - L \frac{d}{dt} i - R i - k_{\theta} \theta_1 = 0$$