

CSE 141 Lab #2: 9-bit CPU – Register file, ALU, and fetch unit


due Friday, November 1

In this lab assignment, you will design the register file, ALU (arithmetic logic unit) and the fetch unit for your CPU. For this and future designs, I want the *highest* level of your design to be schematic (like the handout). Anything below that can be schematic or verilog (preferably System Verilog). For example, to generate this example, I have a project composed of one .bdf file (shown), and two verilog .v files (ALU.v and regfile.v). The verilog files implement the symbols included in the .bdf file. Everyone will use the Altera Quartus II tools, so we can compare timing between groups. Configure it for the Cyclone II family, device EP2C35F672C6.

You will not connect everything together yet; you will demonstrate each separately through schematic and timing printouts. For demonstration purposes, I have connected the register file and ALU – you may do the same if you'd like.

You will have an ALU and register file, possibly something like the accompanying schematic. The one shown here is simple and not necessarily reflective of what you will be designing. In this picture, the ALU has two 8-bit inputs, an 8-bit output, some control bits. It also has a zero signal as an output. My register file has 8 registers (3-bit operand specifiers), can read 2 registers per cycle and write one. Registers are 8 bits wide.

 The fetch unit is the logic responsible for fetching the current instruction from the instruction memory and determining the next program counter (PC). It should look roughly like the following diagram:



The *program counter* is a state element (register). *Instruction ROM* is a ROM memory part that holds your code. It doesn't have to actually hold your code at this point, but it might as well – but it should hold something so we can see the effect of changing PCs. The *next PC logic* takes as input the previous PC and several other signals and calculates the next PC value. The inputs to the next PC logic are: *start* – when asserted during a clock edge, it sets the PC to zero or the starting address of your program (note – if you store all three programs in one ROM, you'll have to do this a little differently). *branch* – when asserted it indicates that the prior instruction was a branch. *taken* – when the instruction is a branch, this signal when asserted indicates the branch was resolved as taken. On non-branch instructions, the next PC should be PC+1 (regardless of the value of taken). For branch instructions, the new PC is either PC+1

(branch not taken) or *target* (branch taken). If your branches are ALWAYS PC-relative, then you can redefine *target* to be a signed distance rather than an absolute address if you want. Make sure you tell us this is what you're doing. Otherwise, just do it as I described.

You will demonstrate each element of your design in two ways. First, with schematics such as the one shown. Obviously, you must also show all relevant internal circuits. That will either be further schematics or (system) verilog code. Second, you must demonstrate correct operation of all ALU operations, register file functionality, and fetch unit functions with timing diagrams. An example of a (partial) timing diagram is also included; yours will be longer. The timing diagrams, for example, should demonstrate all ALU operations (this includes math to support load address computation, or any other computation required by your design), each with a couple of interesting inputs. Make sure corner/unusual cases are demonstrated, if relevant. If you support instructions that do multiple computations at the same time, you need to demonstrate them happening at the same time unless you've already determined that they will happen in different pipeline stages. Note that you're demonstrating ALU operations, not instructions. So for example, instructions that do no computation (e.g., branch to address in register) need not be demonstrated. There will also be a timing diagram for the fetch unit, showing it doing everything interesting. The schematics and timing diagrams will be difficult for us to understand without a *great deal* of annotation. Good organization and use of hierarchical design also help.

The lab report will contain the following:

1. Introduction and general comments. Overview of report.
2. Summarize your ISA from Lab 1 (operations supported, with full detailed descriptions).
3. A listing of ALU operations you will be demonstrating, including the instructions they are relevant to. Also, a description of the register file functionality needed.
4. Full schematics, hierarchically organized.
5. Timing diagrams. It should be clear everything works. If your presentation leaves doubt, we'll assume it doesn't.

Answer the following questions:

6. How many (and what) ALU operations do you support?
7. Will your ALU be used for non-arithmetic instructions (e.g., address calculation, branches)? If so, how does that complicate your design?
8. Name one thing you could have done differently in your ISA design to make your ALU design easier.
9. Name one thing you could have done differently in your ISA design to make your register file design easier.
10. What is your most complex instruction, from the standpoint of the ALU?
11. Now that your ALU is designed, are there any instructions that would be particularly straightforward to add given the hardware that is already there?
12. Is there anything you could have done in your ISA to make your fetch unit design job easier?
13. Give a qualitative description of your expected (pipelined) cycle time, assuming it is dictated by the ALU design – relatively fast, average, slowwww... (or better, it is the sum of ... access time plus ... plus ...). Explain. What could you do to improve cycle time?