

ECE 715

System on Chip Design and Test

Lecture 5: SoC Physical Design Issues



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI



Design Challenges



 
1. Non-scalable global wire delay
2. Moving signals across a large die within one clock cycle is not possible.
3. Current interconnection architecture- Buses are inherently non-scalable.
4. Transmission of digital signals along wires is not reliable.



Interconnect Scaling Effects



- Dense multilayer metal increases coupling capacitance




- Long/narrow line widths further increases resistance of interconnect



Effect of Advanced Interconnect


 
SPEED / PERFORMANCE ISSUE *The Technical Problem*



Effect of Wire Scaling on Delay




- What happens to wire delay?
- Many people claim that wire delay goes up, as shown in the famous plot from the 1995 SIA roadmap
- But it depends on how you scale the wires and which wires you are talking about.
- In a technology shrink ($s < 1$)
- There are really two types of wires
 - a. Wires that scale L directly by s ,
 - b. Wires of constant percentage of die size, the global wires of the increasing complex chips
- Delay is different for these two cases as shown here:

 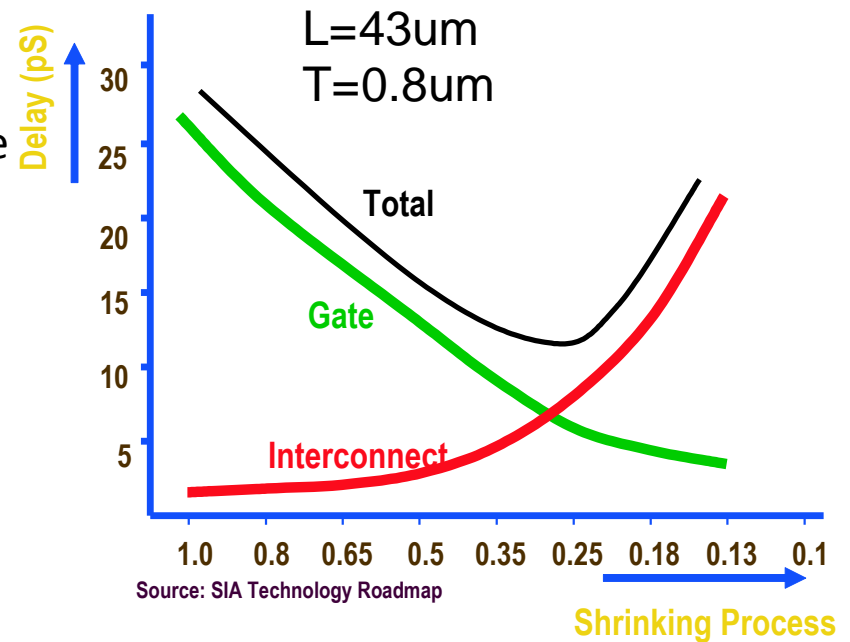

Global Wire Delay

➤ Global wires

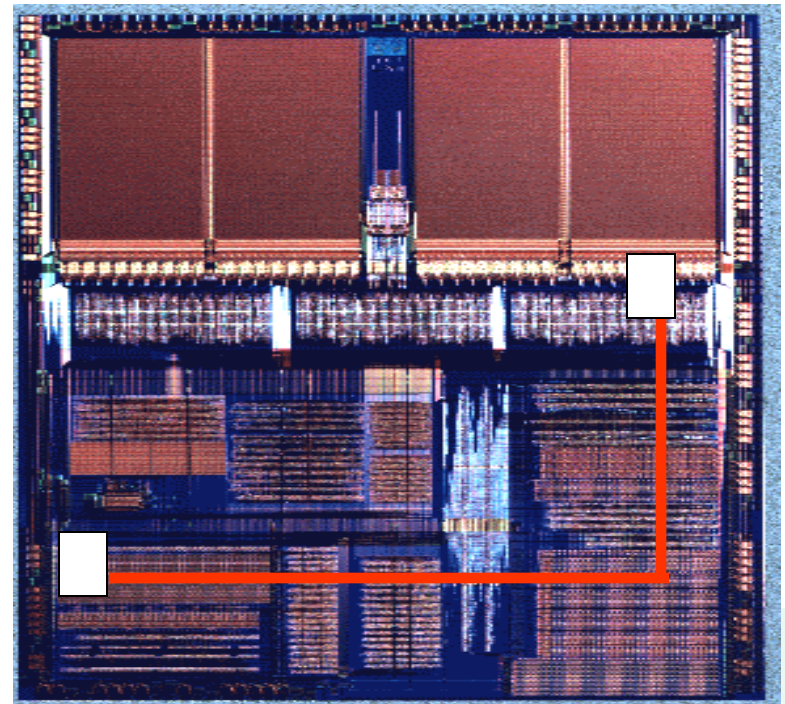- Non-scalable delay
- Delay exceeds one clock cycle



Wire Modeling






Wires are a distributed RC circuit

- Wire has r = resistance/mm and c = capacitance/mm


How should you model the interconnect for hand calc?

   Use a simple L, Π , or T model assuming $C = cL$ and $R = rL$



- One of the three models above is not useful for distributed RC modeling
- Even with proper modeling, we still have to deal with RC trees

Elmore Delay

 


- For a general RC ladder finding the first-order delay is easy!
Delay = $R1 C1 + (R1 + R2) C2 + (R1 + R2 + R3) C3$
i.e., Delay = $\sum \text{Cap}_i \times (\text{resistance from Cap}_i \text{ to source})$
= ELMORE DELAY
- Notice this gives the right answer if all C's but one are zero, or all R's but one are zero
- However, in general, it is only a good delay estimate at the end of the tree

Elmore Delay



$$\tau_i = \sum R_{ik} \sum C_k$$

 

- C_k = every capacitance in the network in sequence
- R_{ik} = common resistance in path between source and node i and source and node k

$$\tau_1 = R1C1 + R1C2 + R1C3$$


$$\tau_2 = R1C1 + (R1+R2)C2 + R1C3$$

$$\tau_3 = R1C1 + R1C2 + (R1+R3)C3$$

Delay of a wire




 - What is the delay along the distributed line as a function on length L ?



$$\begin{aligned} \text{Use Elmore delay} &= (r \Delta L)(c \Delta L) + 2(r \Delta L)(c \Delta L) + \dots + N(r \Delta L)(c \Delta L) \\ &= (\Delta L)^2 rc(1 + 2 + \dots + N) \\ &= (\Delta L)^2 rc(N)(N+1)/2 \approx (\Delta L)^2 rcN^2 \\ &= L^2 rc/2 = RC/2 \text{ (according to Elmore)} \\ &\approx 0.4rcL^2 \text{ (measured)} \quad \text{Note that delay is proportional to length}^2 \end{aligned}$$


FO4 vs. Wire Delay

 

Buffer Insertion for Long Wires



 - Make Long wires into short wires by inserting buffers periodically. Divide interconnect into N sections as follows:



$$R_{\text{eff}} = R_{\text{eqn}}/M \quad C_{\text{self}} = C_j 3W * M \quad C_{\text{fanout}} = C_g 3W * M \quad R_w = R_{\text{int}} L/N \quad C_w = C_{\text{int}} L/N$$

- Then delay through buffers and interconnect is given by:

$$t_p = N * [R_{\text{eff}}(C_{\text{self}} + C_w/2) + (R_{\text{eff}} + R_w)(C_w/2 + C_{\text{fanout}})]$$

- What is the optimal number of buffers?

$$\text{Find } N \text{ such that } \partial t_p / \partial N = 0 \Rightarrow N \approx \text{sqrt}(0.4 R_{\text{int}} C_{\text{int}} L^2 / t_{\text{pbuf}})$$

$$\text{where } t_{\text{pbuf}} = R_{\text{eff}}(C_{\text{self}} + C_{\text{fanout}})$$

- What size should the buffers be?

$$\text{Find } M \text{ such that } \partial t_p / \partial M = 0 \Rightarrow M = \text{sqrt}((R_{\text{eqn}}/C_g 3W)(C_{\text{int}}/R_{\text{int}}))$$

Issues in Buffer Insertion




- Even number of repeaters needed to avoid logic inversion
- Better strategy to optimize the delay-power product
- Repeater for global wires require many via cuts from the upper-layer wires all the way down to the substrate
- Floorplanning
- Area and power
- Repeated wires offer increased bandwidth



Gate Delay Scaling

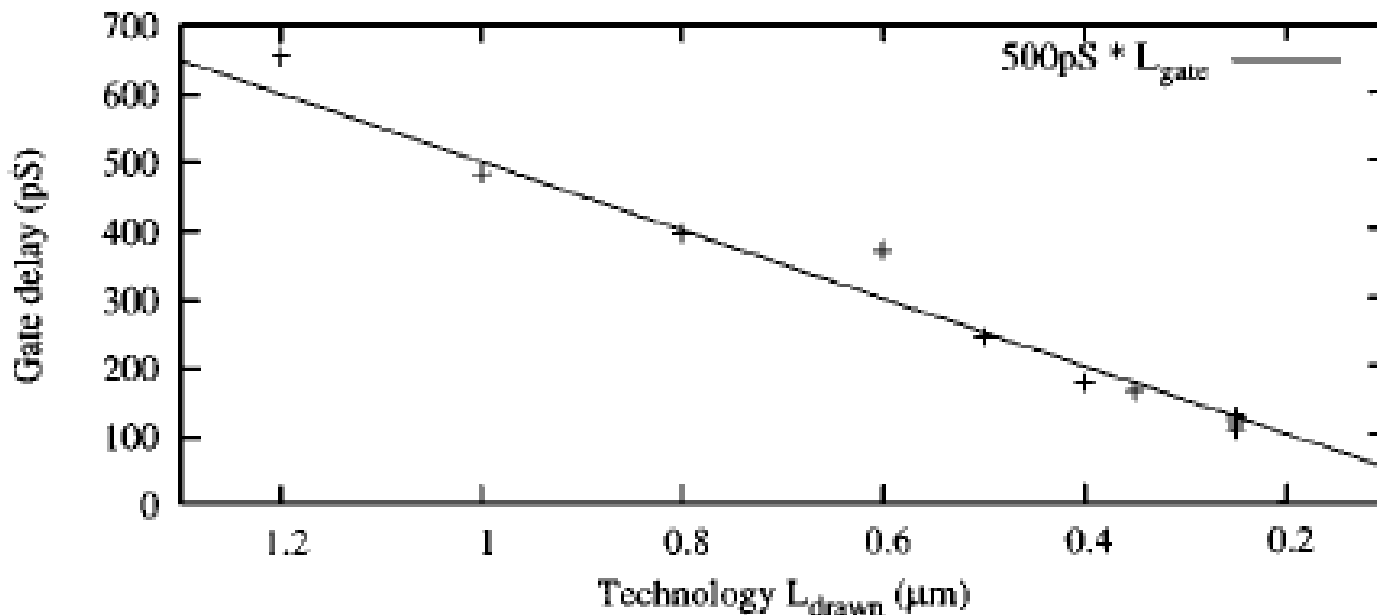- Gate delay has scaled almost linearly.
- Gate and Diffusion capacitance also scale nicely



Wire Scaling

- Resistance: Resistance grows under scaling, since the width and height both scale down


L_drawn	0.18 um	0.13 um	0.10 um	0.07 um	0.05 um	0.035 um
Semi-global pitch, um	0.36	0.26	0.20	0.14	0.10	0.07
Global pitch, um	0.72	0.52	0.40	0.28	0.20	0.14
Chip edge, mm	19	20.7	22.8	24.9	27.4	30.1

Detail analysis of capacitance in later classes

Delay and Bandwidth

• Classification of wires

 - Connects gates locally within blocks, when devices and blocks get smaller, these wires get shorter
- Connects blocks together, spanning significant portion of the die




Delay and Bandwidth (Cont'd)

- Wires that scale in length
 - Delay scales with technology
 - Wires span block of 50k gates
- Wires that do not scale in length
 - Increasing delay disparity with gates
 - Relative to gate delay roughly doubles each generation




Global wire delay



 


- Global wires limit the system performance


Uniformly Repeated Lines

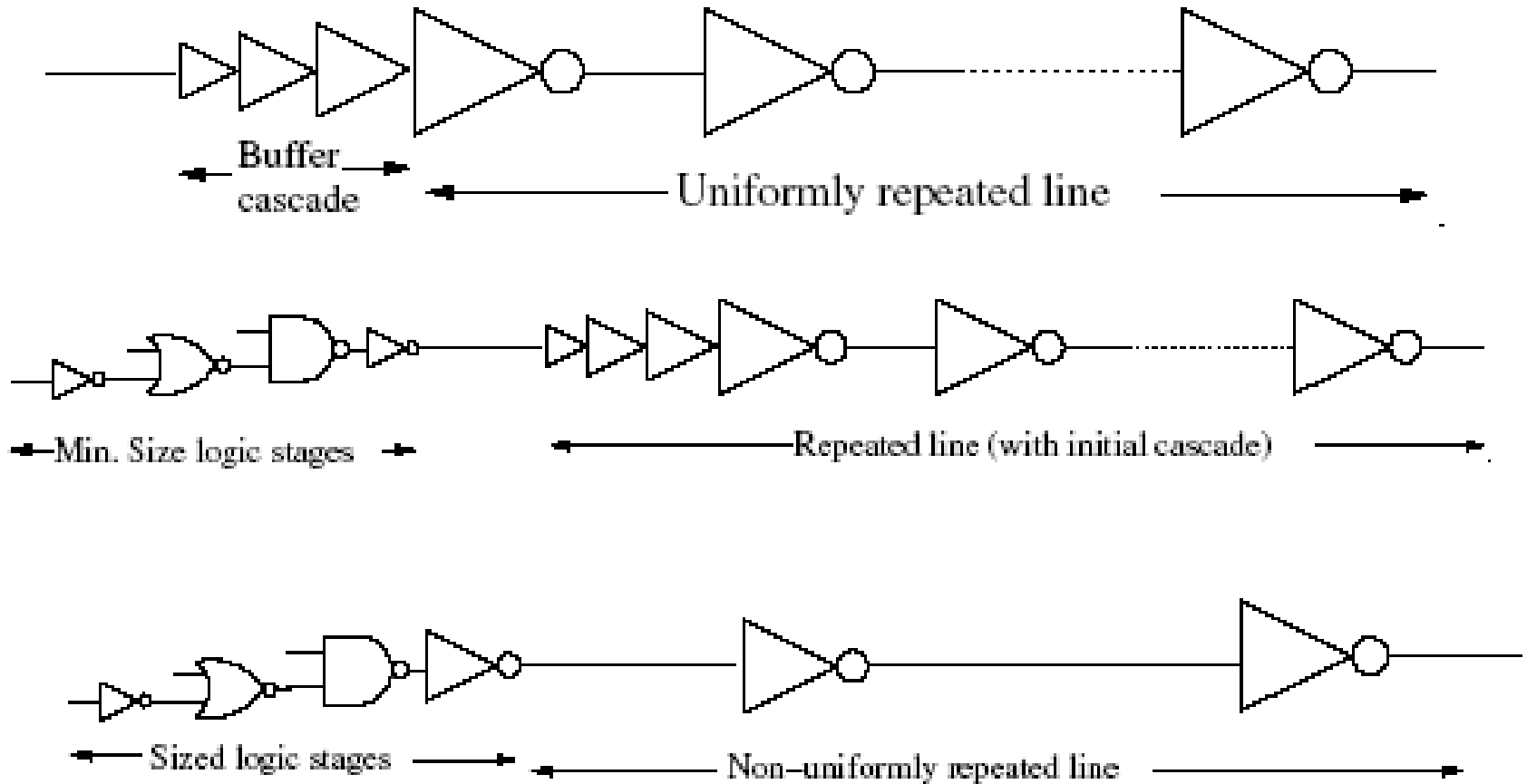

Non-uniform Buffer Insertion

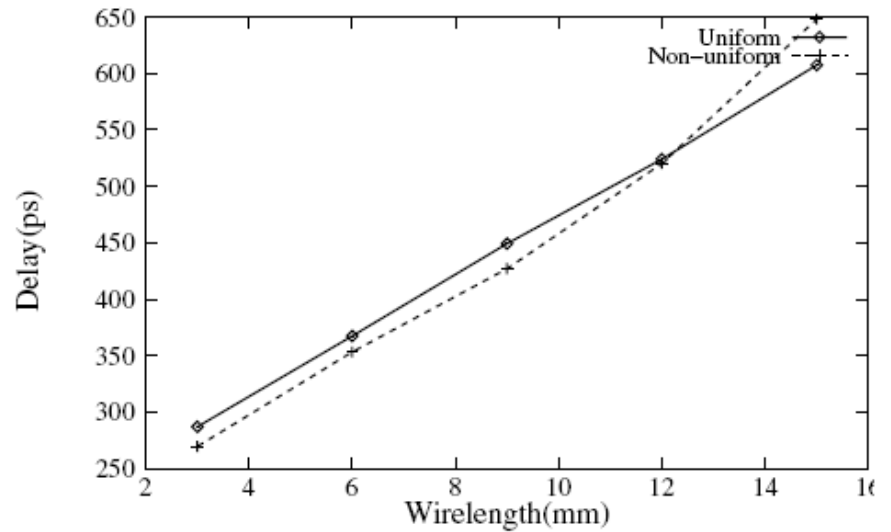  

Non-uniform Buffer Insertion (Cont'd)

 

- Gain in power consumption is due to less number of buffers

Summary

- Single synchronous clock region will span only a small fraction of the chip area
- We should not try to distribute a single low power clock all along the whole chip
- The whole SoC needs to be divided into multiple functional islands with independent frequency
- Synchronization of signals crossing multiple clock boundary is important



Discussion on Project Ideas

