Digital VLSI design

Lecture 2:

Complementary Metal Oxide Semiconductor (CMOS) Chips



INDRAPRASTHA INSTITUTE of INFORMATION TECHNOLOGY **DELHI**



What will we learn?



- How integrated circuits work
- How to design chips with millions of transistors
 - Ways of managing the complexity
 - Use of tools to speed up the design process
- Identifying performance bottlenecks
- Ways to speeding up circuits
- Making sure the designs are correct
- Making the chips testable after manufacturing
- Other issues: effect of technologies, reducing power consumption etc.

Learning general principles



- Chip design involves optimization, tradeoffs
- Need the ability to work as part of a group
- Technology changes fast, so it is important to understand the general principles which would span technology generations
- Systems are implemented using building blocks (which may be technology-specific)

Lot of work in course, but we will learn a lot

Agenda



- How to build your own simple CMOS chip
 - CMOS transistors
 - Building logic gates from transistors
 - Transistor layout and fabrication (Self-study)
- Rest of the course: How to build a good CMOS chip

- Note:
- This course will not cover semiconductor physics
- We will design VLSI circuits knowing the electrical behavior of the transistor

Silicon Lattice



- Transistors are built on a silicon substrate
- Silicon is a Group IV material
- Forms crystal lattice with bonds to four neighbors

Dopants



- Silicon is a semiconductor
- Pure silicon has no free carriers and conducts poorly
- Adding dopants increases the conductivity
- Group V: extra electron (n-type)
- Group III: missing electron, called hole (p-type)


p-n Junctions



- A junction between p-type and n-type semiconductor forms a diode.
- Current flows only in one direction

p-type n-type


anode cathode

 

nMOS Transistor



 - Four terminals: gate, source, drain, body
- Gate oxide body stack looks like a capacitor
 - Gate and body are conductors
 - SiO₂ (oxide) is a very good insulator
 - Called metal oxide semiconductor (MOS) capacitor
 - Even though gate is no longer made of metal* source Gate Drain




^{*} Metal gates are returning today!

nMOS Operation



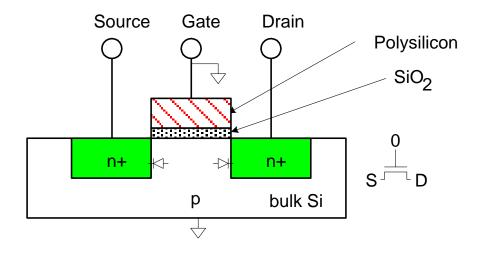
- Body is usually tied to ground (0 V)
- When the gate is at a low voltage:
 - P-type body is at low voltage
 - Source-body and drain-body diodes are OFF
 - No current flows, transistor is OFF



nMOS Operation Cont.



 
- When the gate is at a high voltage:
 - Positive charge on gate of MOS capacitor
 - Negative charge attracted to body
 - Inverts a channel under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



pMOS Transistor



 - Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior



Power Supply Voltage




- GND = 0 V
- In 1980's, $V_{DD} = 5V$
- V_{DD} has decreased in modern processes
 - High V_{DD} would damage modern tiny transistors
 - Lower V_{DD} saves power
- $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, ...$

Transistors as Switches




 
- We can view MOS transistors as electrically controlled switches
- Voltage at gate controls path from source to drain




CMOS Inverter



 

 


 

CMOS NAND Gate




Α	В	Υ
0	0	
0	1	
1	0	
1	1	
)—)—

 


CMOS NOR Gate



Α	В	Υ
0	0	1
0	1	0
1	0	0
1	1	0

 

 

3-input NAND Gate



- Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0

CMOS Fabrication




- CMOS transistors are fabricated on silicon wafer
- Lithography process similar to printing press
- On each step, different materials are deposited or etched
- Easiest to understand by viewing both top and cross-section of wafer in a simplified manufacturing process

Inverter Cross-section



 
- Typically use p-type substrate for nMOS transistors
- Requires n-well for body of pMOS transistors



Well and Substrate Taps



 
- Substrate must be tied to GND and n-well to V_{DD}
- Metal to lightly-doped semiconductor forms poor connection called Shottky Diode
- Use heavily doped well and substrate contacts / taps



Inverter Mask Set



 
- Transistors and wires are defined by masks
- Cross-section taken along dashed line




Detailed Mask Views



 - Six masks
 - n-well
 - Polysilicon
 - n+ diffusion
 - p+ diffusion
 - Contact
 - Metal



 

Fabrication



- Chips are built in huge factories called fabs
- Contain clean rooms as large as football fields



Courtesy of International Business Machines Corporation. Unauthorized use not permitted.

Fabrication Steps



- Start with blank wafer
- Build inverter from the bottom up
- First step will be to form the n-well
 - Cover wafer with protective layer of SiO₂ (oxide)
 - Remove layer where n-well should be built
 - Implant or diffuse n dopants into exposed wafer
 - Strip off SiO₂

p substrate

Oxidation



- Grow SiO₂ on top of Si wafer
 - 900 1200 C with H₂O or O₂ in oxidation furnace

p substrate

Photoresist




- Spin on photoresist
 - Photoresist is a light-sensitive organic polymer
 - Softens where exposed to light

	Photoresist			
	SiO ₂			
p substrate				

Lithography



 - Expose photoresist through n-well mask
- Strip off exposed photoresist



Etch




- Etch oxide with hydrofluoric acid (HF)
 - Seeps through skin and eats bone; nasty stuff!!!
- Only attacks oxide where resist has been exposed

		Photores	sist
p substrate			

Strip Photoresist



 
- Strip off remaining photoresist
 - Use mixture of acids called piranah etch
- Necessary so resist doesn't melt in next step



n-well



 - n-well is formed with diffusion or ion implantation
- Diffusion
 - Place wafer in furnace with arsenic gas
 - Heat until As atoms diffuse into exposed Si
- Ion Implanatation
 - Blast wafer with beam of As ions
 - Ions blocked by SiO₂, only enter exposed Si



Strip Oxide




- Strip off the remaining oxide using HF
- Back to bare wafer with n-well
- Subsequent steps involve similar series of steps

n well p substrate

Polysilicon



 
- Deposit very thin layer of gate oxide
 - < 20 Å (6-7 atomic layers)
- Chemical Vapor Deposition (CVD) of silicon layer
 - Place wafer in furnace with Silane gas (SiH₄)
 - Forms many small crystals called polysilicon
 - Heavily doped to be good conductor



Polysilicon Patterning



 
Use same lithography process to pattern polysilicon



Self-Aligned Process



 - Use oxide and masking to expose where n+ dopants should be diffused or implanted
- N-diffusion forms nMOS source, drain, and n-well contact




N-diffusion



- Pattern oxide and form n+ regions
- Self-aligned process where gate blocks diffusion

  Polysilicon is better than metal for self-aligned gates because it doesn't melt during later processing






N-diffusion cont.



 
- Historically dopants were diffused
- Usually ion implantation today
- But regions are still called diffusion



N-diffusion cont.



 
Strip off oxide to complete patterning step



P-Diffusion



 
 Similar set of steps form p+ diffusion regions for pMOS source and drain and substrate contact



Contacts



 
- Now we need to wire together the devices
- Cover chip with thick field oxide
- Etch oxide where contact cuts are needed



Metalization



 - Sputter on aluminum over whole wafer
- Pattern to remove excess metal, leaving wires



Layout




- Chips are specified with set of masks
- Minimum dimensions of masks determine transistor size (and hence speed, cost, and power)
- Feature size f = distance between source and drain
 - Set by minimum width of polysilicon
- Feature size improves 30% every 3 years or so
- Normalize for feature size when describing design rules
- Express rules in terms of $\lambda = f/2$
 - E.g. λ = 0.3 μ m in 0.6 μ m process

Simplified Design Rules




Conservative rules to get you started

 



Inverter Layout



 - Transistor dimensions specified as Width / Length
 - Minimum size is $4\lambda / 2\lambda$, sometimes called 1 unit
 - In f = 0.6 μ m process, this is 1.2 μ m wide, 0.6 μ m long



 

 

Summary



- MOS transistors are stacks of gate, oxide, silicon
- Act as electrically controlled switches
- Build logic gates out of switches
- Draw masks to specify layout of transistors

 Now you know everything necessary to start designing schematics and layout for a simple chip!

CMOS Gate Design



- Activity:
 - Sketch a 4-input CMOS NOR gate