

Digital VLSI design

Lecture 10: Logical Effort




INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI




Computing Logical Effort

 - DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths




$$C_{in} = 3$$

$$g = 3/3$$

 

$$C_{in} = 4$$

$$g = 4/3$$

 

$$C_{in} = 5$$

$$g = 5/3$$

Catalog of Gates



- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

Catalog of Gates




- Parasitic delay of common gates
 - In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

 Example: Ring Oscillator



- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g =$

Electrical Effort: $h =$

Parasitic Delay: $p =$


Stage Delay: $d =$

Frequency: $f_{\text{osc}} =$

 Example: FO4 Inverter



- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$

Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$

Multistage Logic Networks

- Logical effort generalizes to multistage networks
- *Path Logical Effort*


$$G = \prod g_i$$

- *Path Electrical Effort*

$$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$$

- *Path Effort*

$$F = \prod f_i = \prod g_i h_i$$

 

Multistage Logic Networks

- Logical effort generalizes to multistage networks

- *Path Logical Effort*

$$G = \prod g_i$$

- *Path Electrical Effort*

$$H = \frac{C_{out-path}}{C_{in-path}}$$

- *Path Effort*

$$F = \prod f_i = \prod g_i h_i$$

- Can we write $F = GH$?

Paths that Branch



- No! Consider paths that branch:

G =


H =

GH =

h_1 =

h_2 =

F =

 

Branching Effort



- Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
 - $F = GBH$

Multistage Delays



- Path Effort Delay

$$D_F = \sum f_i$$

- Path Parasitic Delay

$$P = \sum p_i$$

- Path Delay

$$D = \sum d_i = D_F + P$$

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is



- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

- How wide should the gates be for least delay?

$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$


$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.

 
Example: 3-stage path



- Select gate sizes x and y for least delay from A to B



Example: 3-stage path

 

Logical Effort

$G =$

Electrical Effort

$H =$

Branching Effort

$B =$

Path Effort

$F =$

Best Stage Effort

$\hat{f} =$

Parasitic Delay

$P =$

Delay

$D =$

Example: 3-stage path

- Work backward for sizes

$y =$

$x =$

