

Digital VLSI design

Lecture 13: Combinational Circuit Design



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI



- Def: Logical effort of a skewed gate for a particular transition is the ratio of the input capacitance of that gate to the input capacitance of an unskewed inverter delivering the same output current for the same transition.
- Skewed gates reduce size of noncritical transistors
 - HI-skew gates favor rising output (small nMOS)
 - LO-skew gates favor falling output (small pMOS)
- Logical effort is smaller for favored direction
- But larger for the other direction

Catalog of Skewed Gates






Inverter




NAND2

NOR2




unskewed

   

HI-skew

   



LO-skew

   

Asymmetric Skew



  
- Combine asymmetric and skewed gates
 - Downsize noncritical transistor on unimportant input
 - Reduces parasitic delay for critical input



Best P/N Ratio



 - We have selected P/N ratio for unit rise and fall resistance ($\mu = 2-3$ for an inverter).
- Alternative: choose ratio for least average delay
- Ex: inverter
 - Delay driving identical inverter
 - $t_{pdf} =$
 - $t_{pdr} =$
 - $t_{pd} =$
 - $dt_{pd} / dP =$
 - Least delay for $P =$




P/N Ratios




- In general, best P/N ratio is sqrt of equal delay ratio.
 - Only improves average delay slightly for inverters
 - But significantly decreases area and power

Inverter


fastest
P/N ratio

 

NAND2

 

NOR2

 

- For speed:
 - NAND vs. NOR
 - Many simple stages vs. fewer high fan-in stages
 - Latest-arriving input
- For area and power:
 - Many simple stages vs. fewer high fan-in stages

Another Example




Size the path G1-G2-G3-G4 in the circuit below using logical effort
Find the minimum delay and give the sizes of the P and N transistors to achieve this delay

Assume that the off-path capacitance is the same as the on-path capacitance for each branch

Input capacitance of Inverter G1 = 3 units.

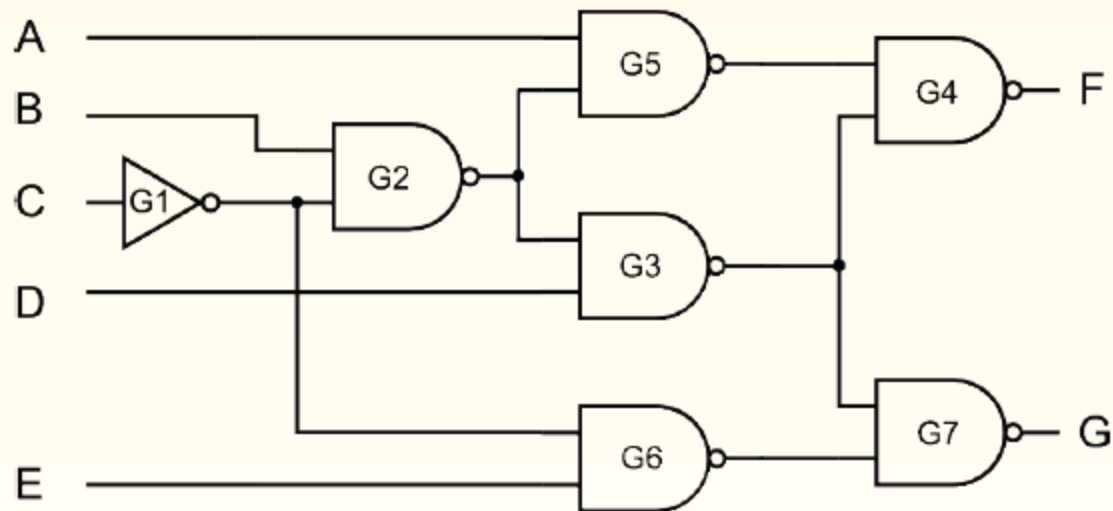Load capacitance driven by Gate G4 = 52 units.



Circuit Families




INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI



- Pseudo-nMOS Logic
- Dynamic Logic
- Pass Transistor Logic


 
- What makes a circuit fast?
 - $I = C \, dV/dt \rightarrow t_{pd} \propto (C/I) \, \Delta V$
 - low capacitance
 - high current
 - small swing
- Logical effort is proportional to C/I
- pMOS are the enemy!
 - High capacitance for a given current
- Can we take the pMOS capacitance off the input?
- Various circuit families try to do this...



Pseudo-nMOS



  
- In the old days, nMOS processes had no pMOS
 - Instead, use pull-up transistor that is always ON
- In CMOS, use a pMOS that is always ON
 - *Ratio* issue
 - Make pMOS about $\frac{1}{4}$ effective strength of pulldown network




Pseudo-nMOS Gates



 
- Design for unit current on output to compare with unit inverter.
- pMOS fights nMOS



Inverter

 

NAND2

 

NOR2

