

# Digital VLSI design

---

## Lecture 14: Circuit Families




INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI



 
# Pseudo-nMOS Gates




- Design for unit current on output to compare with unit inverter.
- pMOS fights nMOS




Inverter

 

NAND2

 


NOR2

 

 
# Pseudo-nMOS Gates


- Design for unit current on output to compare with unit inverter.
- pMOS fights nMOS




Inverter

 

NAND2

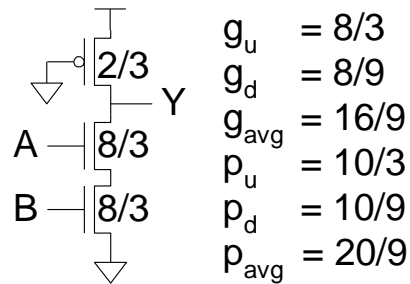

NOR2

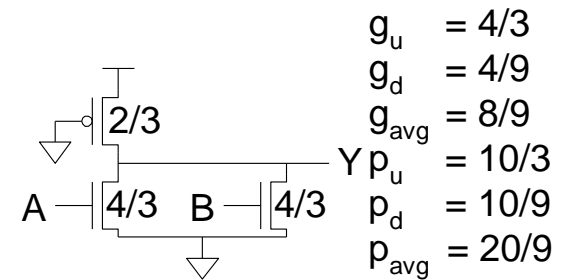

# Pseudo-nMOS Design



- Ex: Design a k-input AND gate using pseudo-nMOS. Estimate the delay driving a fanout of H


- $G = 1 * \frac{1}{n} - \frac{1}{n}$

- $F = G$

- $P = 1$

- $N = 2$


- $D = N$

 
 
# Pseudo-nMOS Power



- Pseudo-nMOS draws power whenever  $Y = 0$ 
  - Called static power  $P = I_{DD} V_{DD}$
  - A few mA / gate \* 1M gates would be a problem
  - Explains why Pseudo-nMOS went extinct
- Use pseudo-nMOS sparingly for wide NORs
- Turn off pMOS when not in use



# Ratio Example



- The chip contains a 32 word x 48 bit ROM
  - Uses pseudo-nMOS decoder and bitline pullups
  - On average, one wordline and 24 bitlines are high
- Find static power drawn by the ROM
  - $I_{\text{on-p}} = 36 \mu\text{A}$ ,  $V_{\text{DD}} = 1.0 \text{ V}$

- Solution:





$$P_{\text{pull-up}} =$$

$$P_{\text{static}} =$$
    
# Dynamic Logic






- *Dynamic* gates uses a clocked pMOS pullup
- Two modes: *precharge* and *evaluate*


   
# The Foot



- What if pulldown network is ON during precharge?
- Use series evaluation transistor to prevent fight.






# Logical Effort




Inverter



unfooted

 



footed

 

NAND2

  


NOR2

  
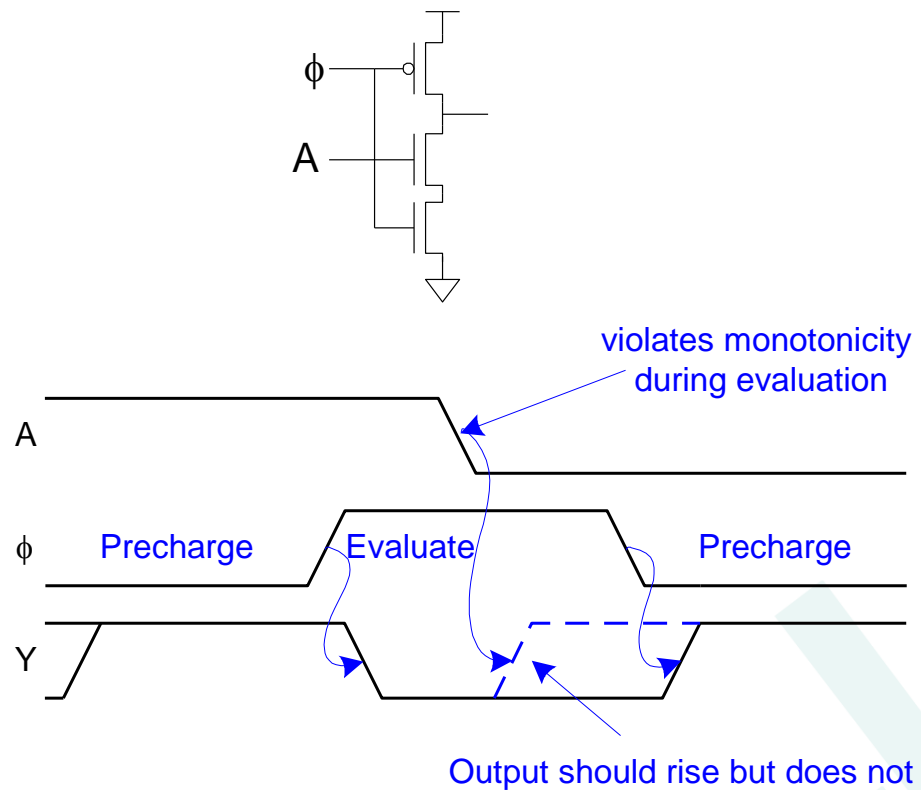
# Monotonicity





- Dynamic gates require *monotonically rising* inputs during evaluation
  - 0 -> 0
  - 0 -> 1
  - 1 -> 1
  - But not 1 -> 0


  
# Monotonicity Woes

- But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!



# Domino Gates



- Follow dynamic stage with inverting static gate
  - Dynamic / static pair is called domino gate
  - Produces monotonic outputs

