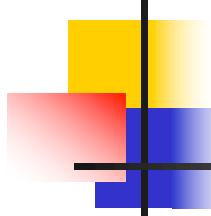


16.480/552

# Intel 80386DX and its Memory Interfaces

The 80386, 80486 and Pentium  
Prof. Yan Luo, UMass Lowell




# Hardware Organization of the Physical Memory Space


---

- Figure 9.20
- Four independent byte-wide banks
  - What is the address range of a bank?
- Address bits are applied to all banks in parallel
- BE bits enable individual bank
- Accessing a byte, word, double word - Figure 9.21(a)-(d)
- Misaligned double-word transfer - Figure 9.24

# Alignment

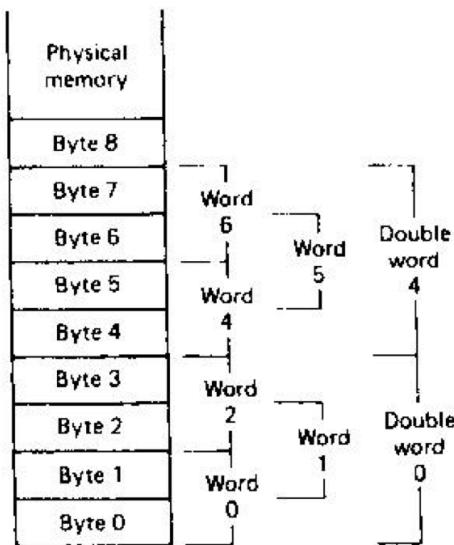

**Figure 9.22** Examples of aligned data words and double words.

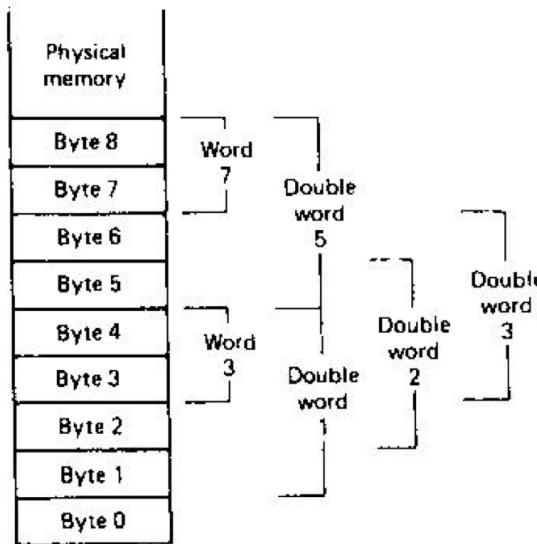

**Figure 9.23** Examples of misaligned data words and double words.

# Transfer of Misaligned Double-Word

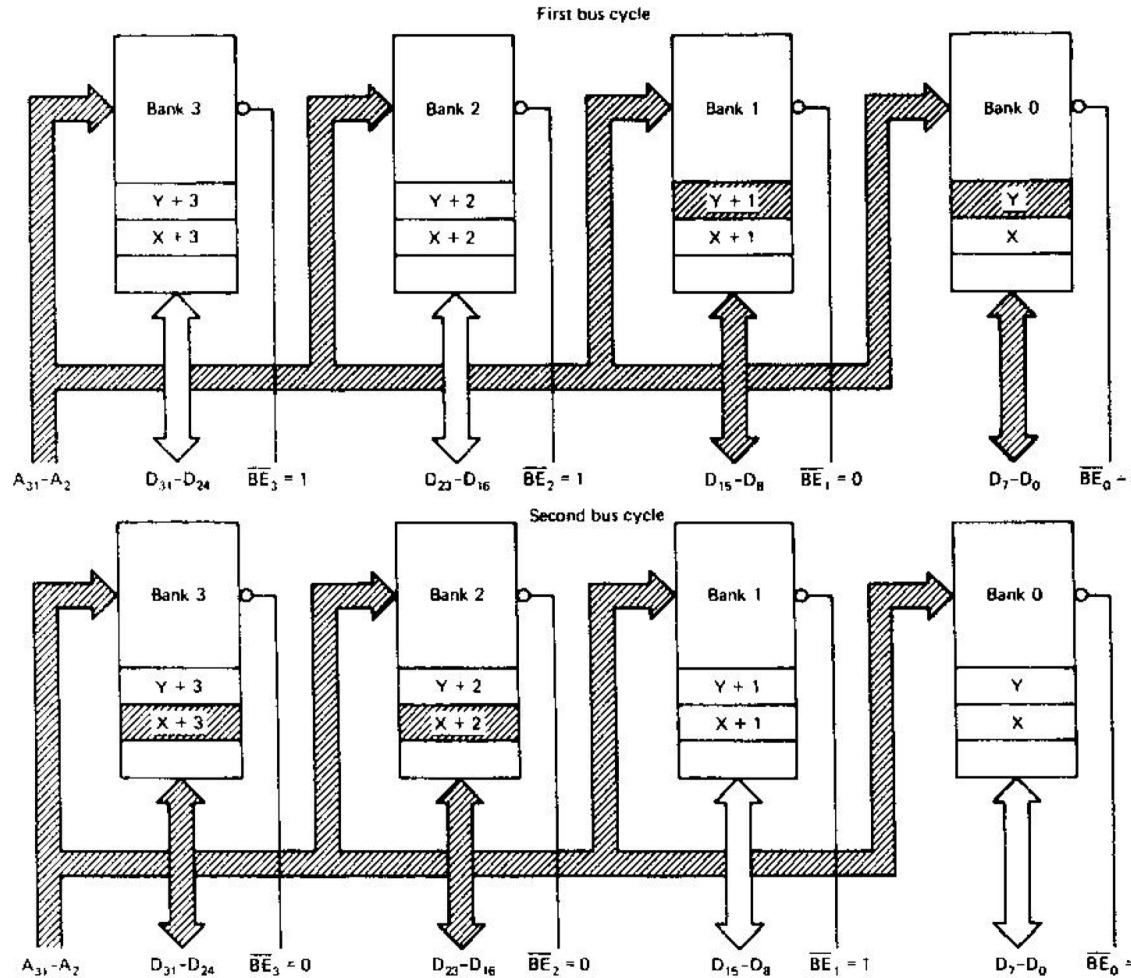


Figure 9.24 Misaligned double-word data transfer.

The 80386, 80486 and Pentium  
Prof. Yan Luo, UMass Lowell

# Memory Interface Block Diagram



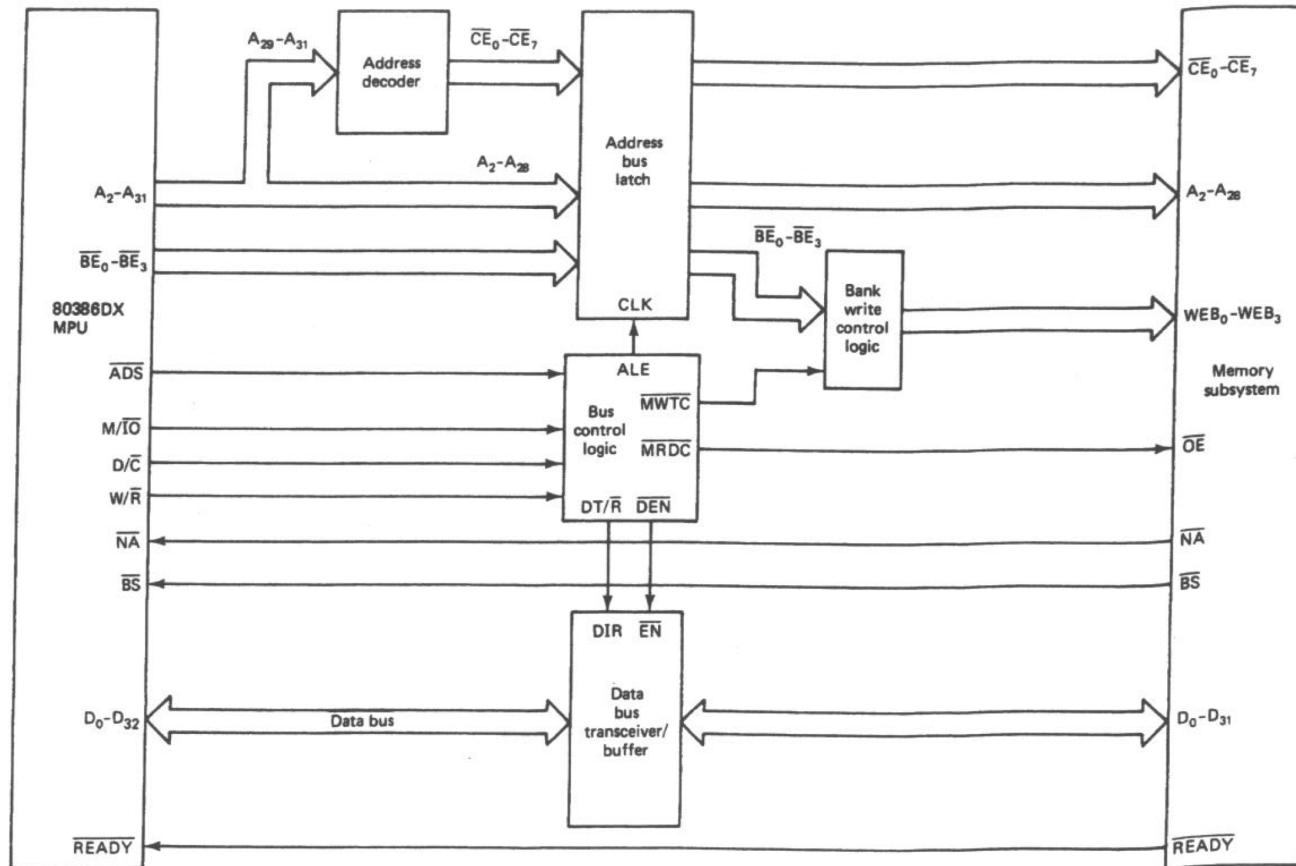


Figure 9.25 Memory interface block diagram.

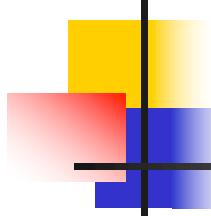

# Memory Interface Circuitry

- Figure 9.25
  - Bus control logic
  - Address bus latches (Fig 9.26, 9.27)
  - Address decoder
  - Bank write control logic
  - Data bus transceiver/buffer (Fig 9.30, 9.31)

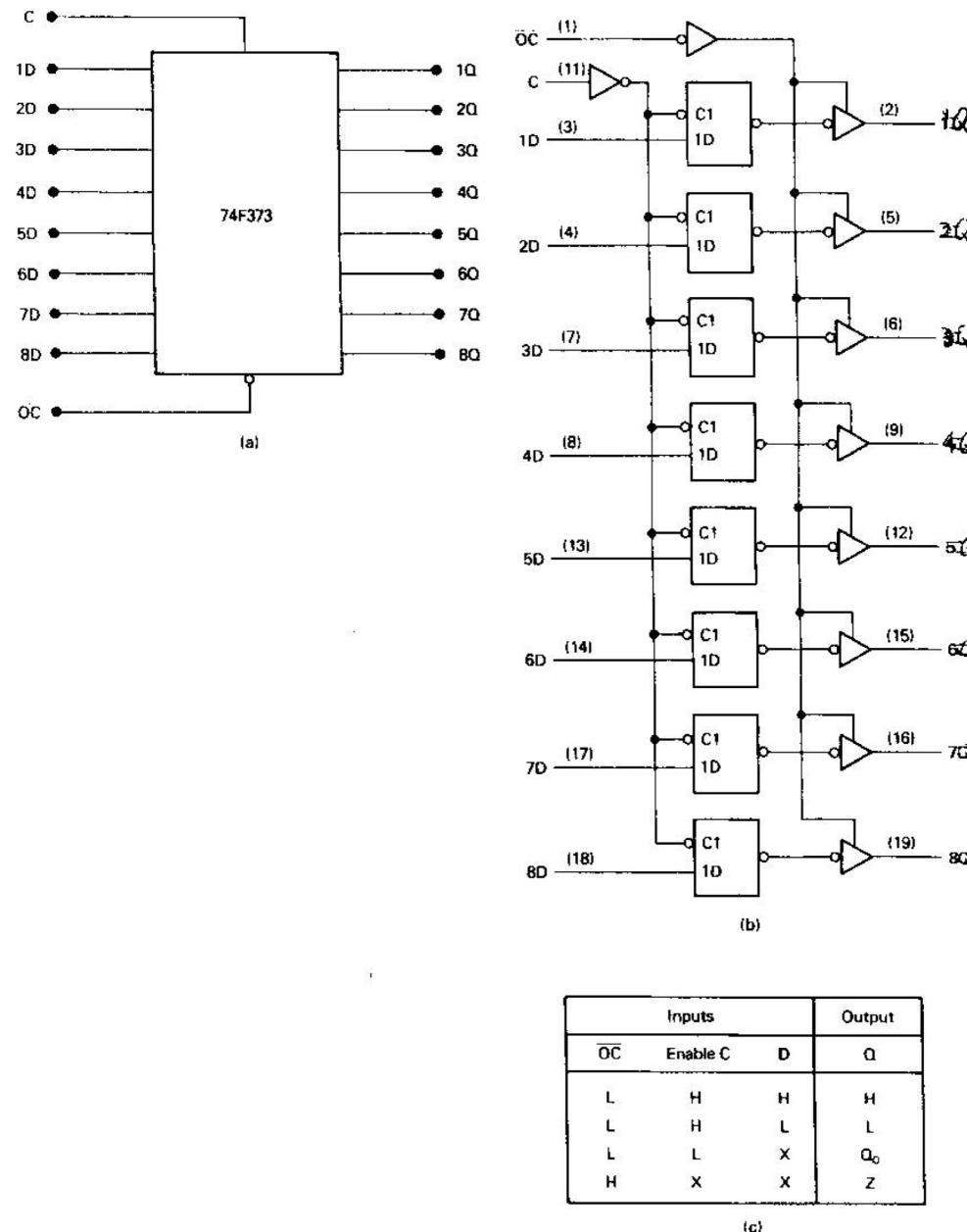

**Figure 9.26** (a) Block diagram of an octal D-type latch. (b) Circuit diagram of the 74F373. (Courtesy of Texas Instruments Incorporated) (c) Operation of the 74F373. (Courtesy of Texas Instruments Incorporated)


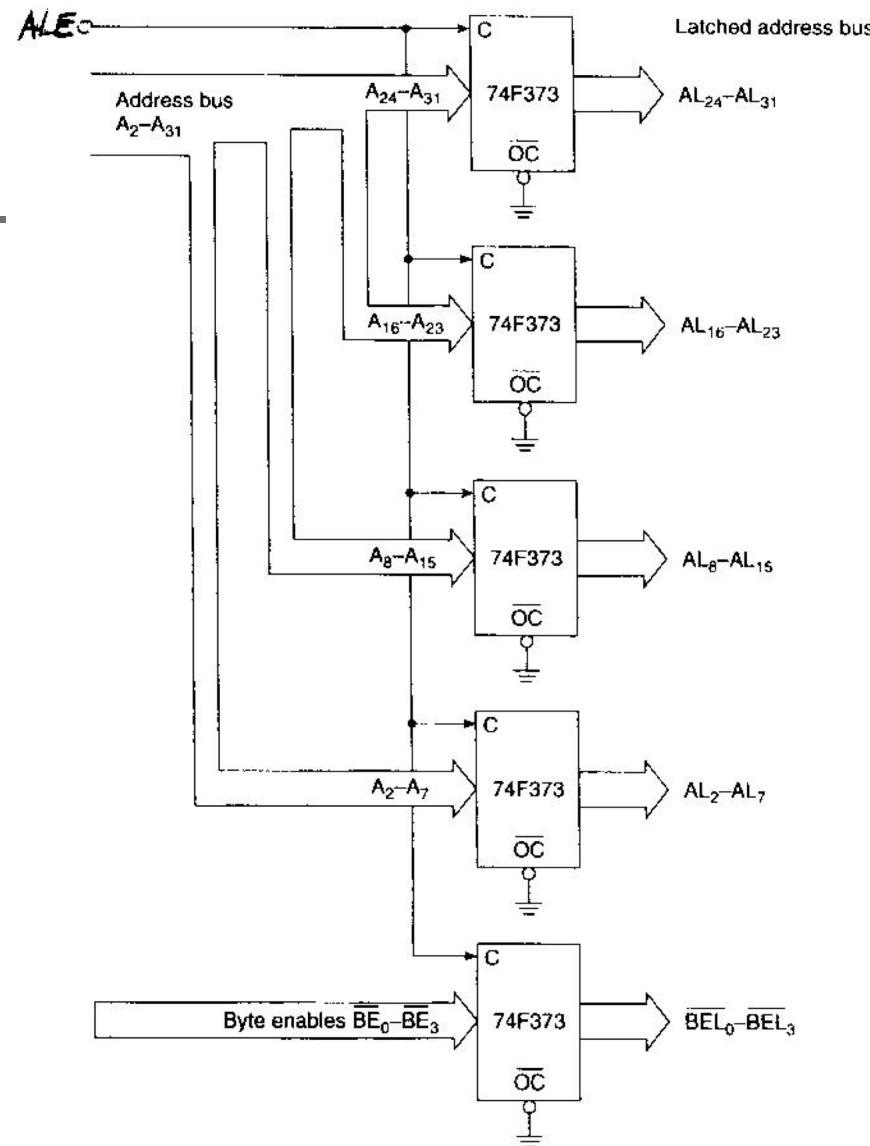


Figure 9.27 Address-latch circuit.

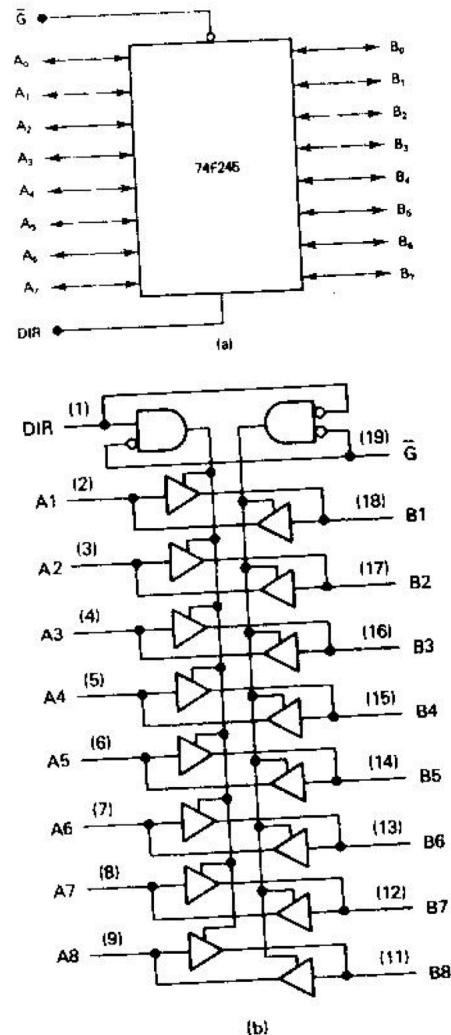

**Figure 9.30** (a) Block diagram of the 74F245 octal bidirectional bus transceiver. (b) Circuit diagram of the 74F245. (Courtesy of Texas Instruments Incorporated)

# Data Bus Transceiver Circuit

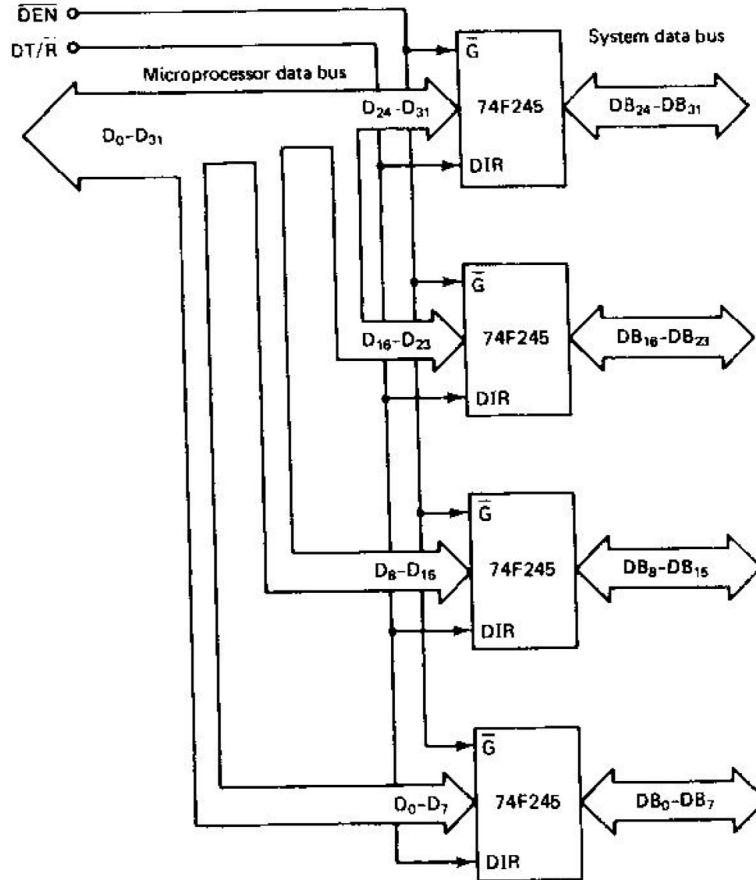


Figure 9.31 Data bus transceiver circuit.

# Decoder



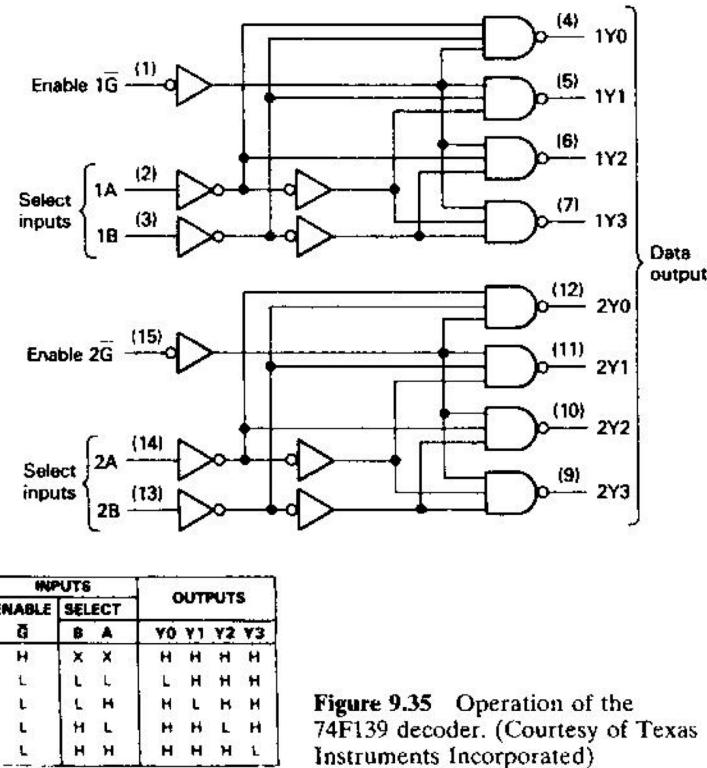


Figure 9.35 Operation of the 74F139 decoder. (Courtesy of Texas Instruments Incorporated)

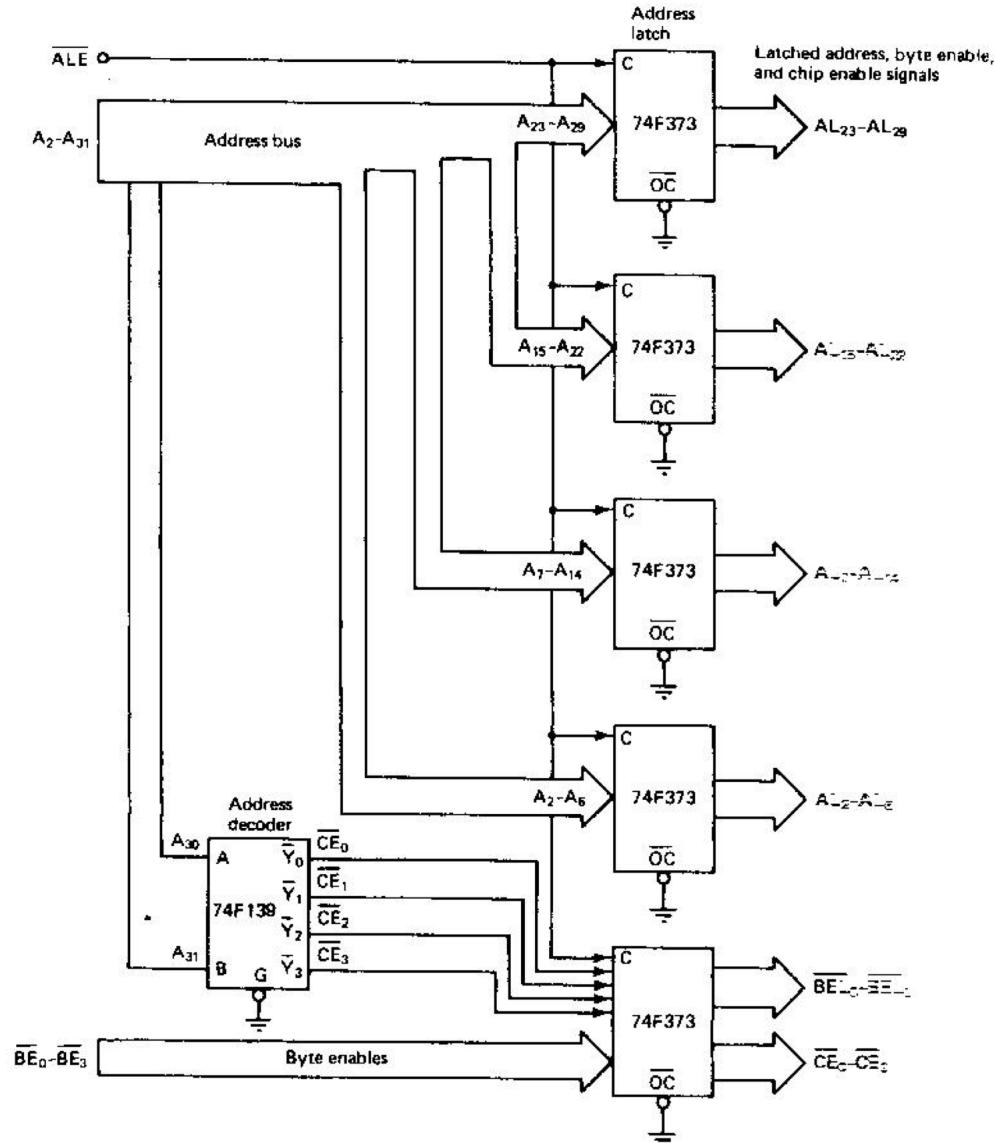


**Figure 9.36** Address decoder/latch circuit.

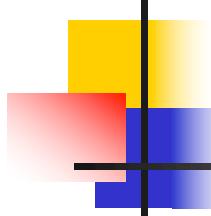The 80386, 80486 and Pentium  
Prof. Yan Luo, UMass Lowell



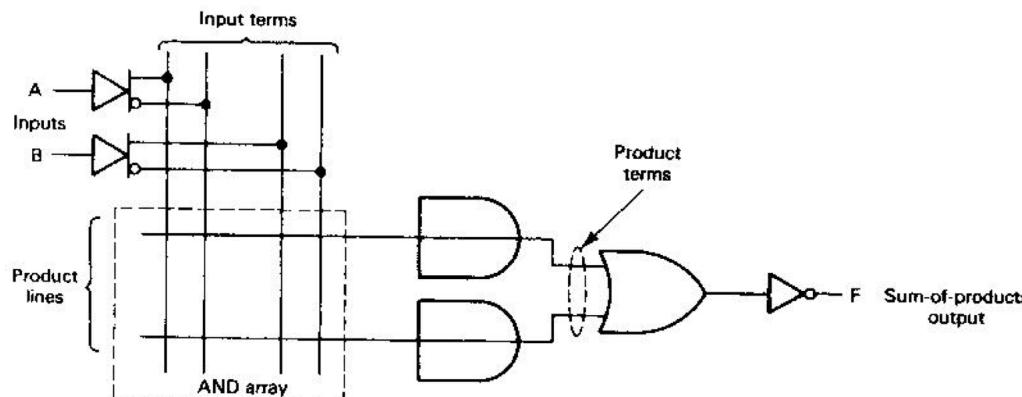
# Programmable Logic Array

- General purpose logic device
- Contains a AND-OR-NOT array of logic gate circuits
- User has the ability to interconnect the inputs to the AND gates of this array
- Technologies
  - Bipolar
  - CMOS (complex, high-speed, low-power)
    - Electrically erasable read-only memory (E<sup>2</sup>ROM)
    - Electrically programmable read only memory (EPROM) – use ultraviolet light to erase
- Figure 9.39 - Architecture of a PLA




(a)

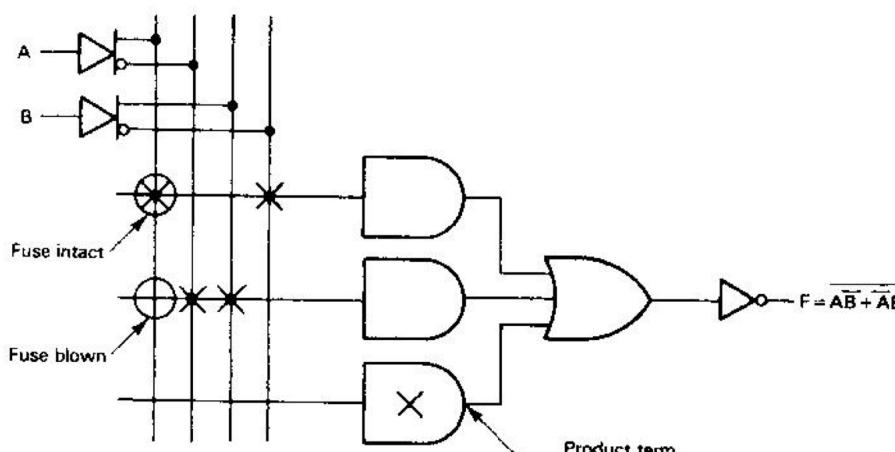


(b)


**Figure 9.39** (a) Basic PLA architecture. (b) Implementing the logic function  $F = (\overline{A}\overline{B} + \overline{A}B)$ .

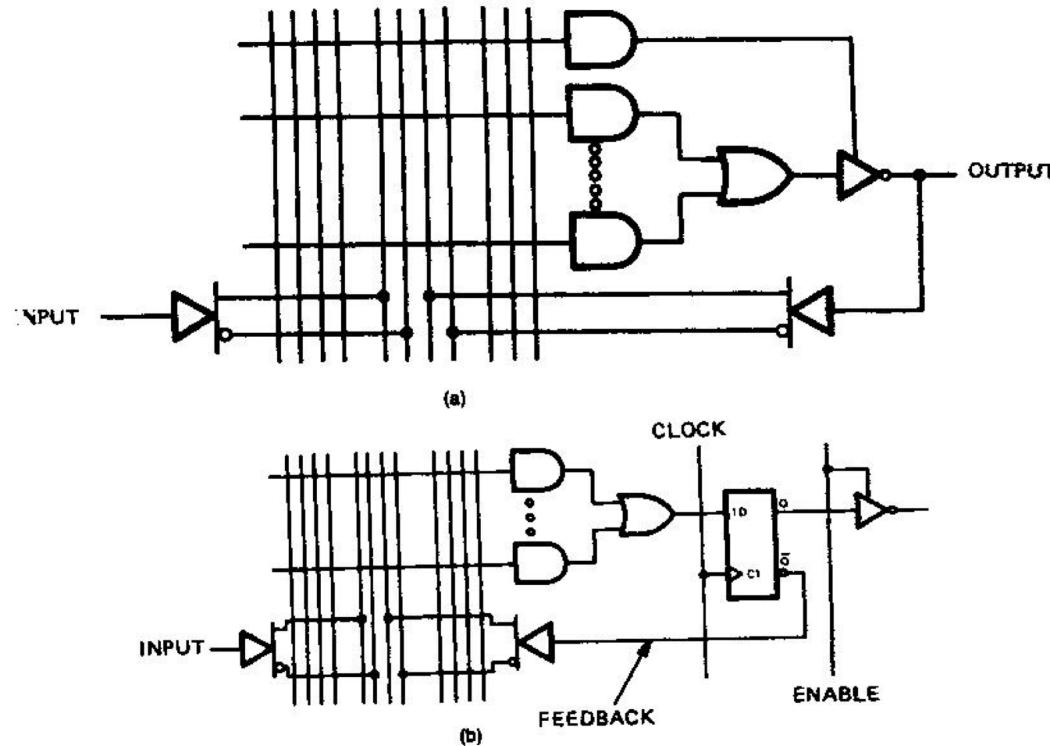

**Figure 9.40** (a) Typical PLA architecture. (Courtesy of Texas Instruments Incorporated) (b) PLA with output latch. (Courtesy of Texas Instruments Incorporated)

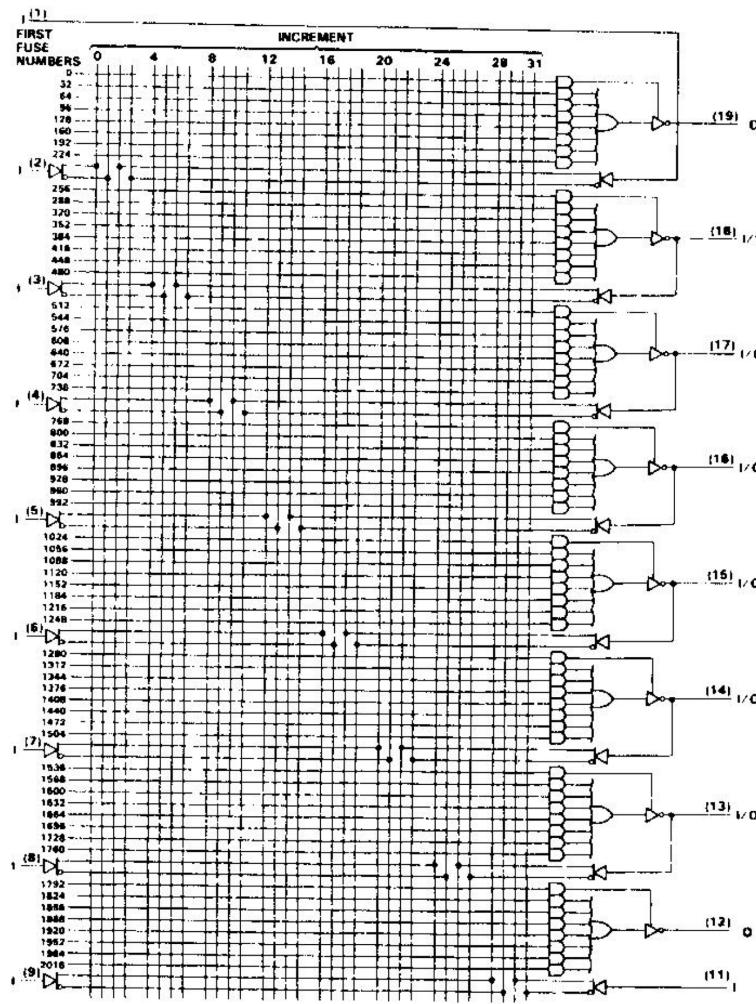


(a)

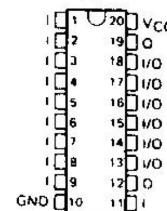


(b)

**Figure 9.41** (a) 16L8 circuit diagram. (Courtesy of Texas Instruments Incorporated) (b) 16L8 pin layout. (Courtesy of Texas Instruments Incorporated)

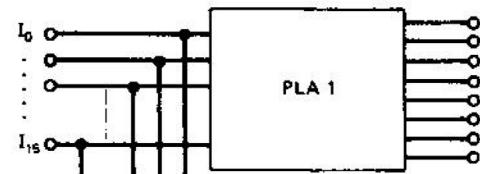


(a)

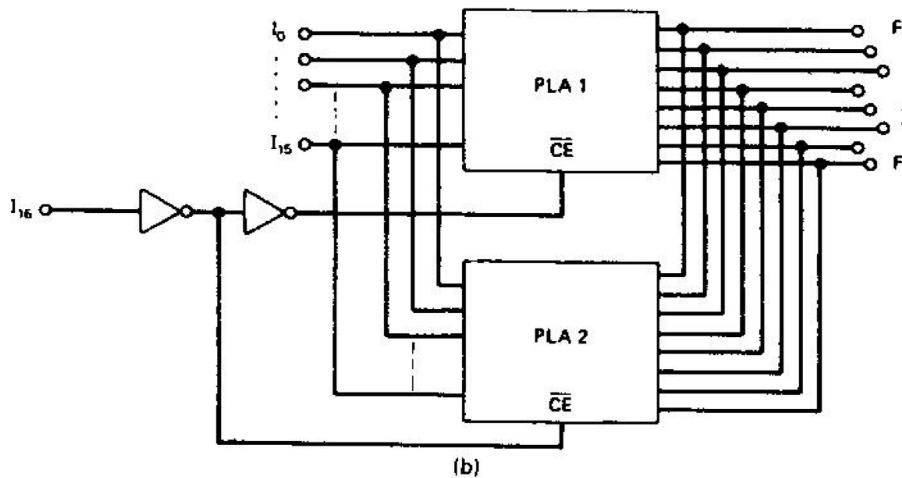

(b)

**Figure 9.45** (a) Expanding output-word length. (b) Expanding input-word length. (Courtesy of Walter A. Triebel)

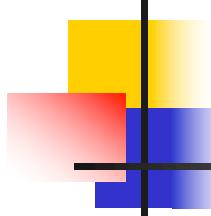

# Programmable Logic Array

---

- Typical PLA architectures
  - Three state output control
  - Output feedback
  - Outputs latched with registers

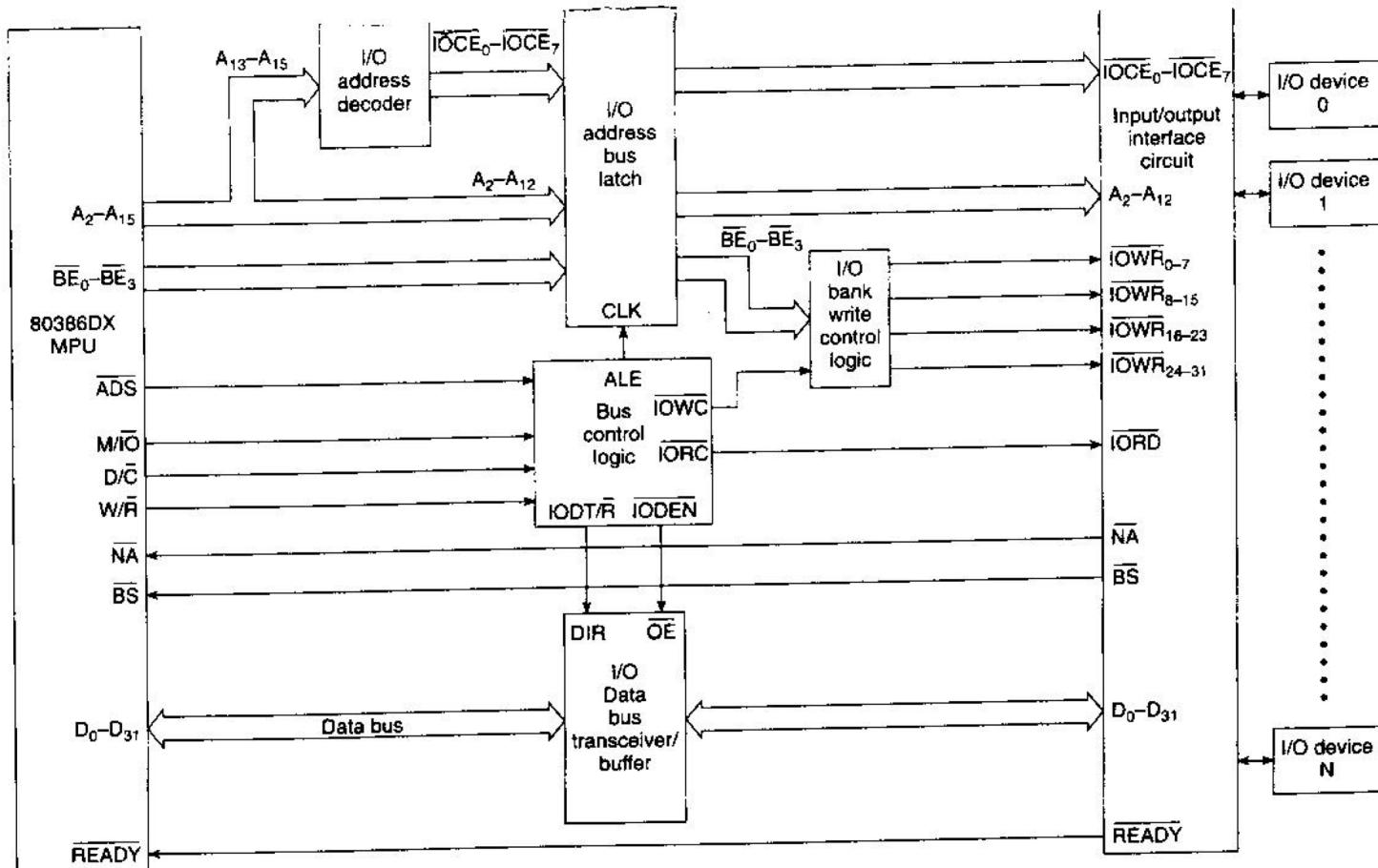


Figure 9.49 Byte, word, and double-word I/O interface block diagram.

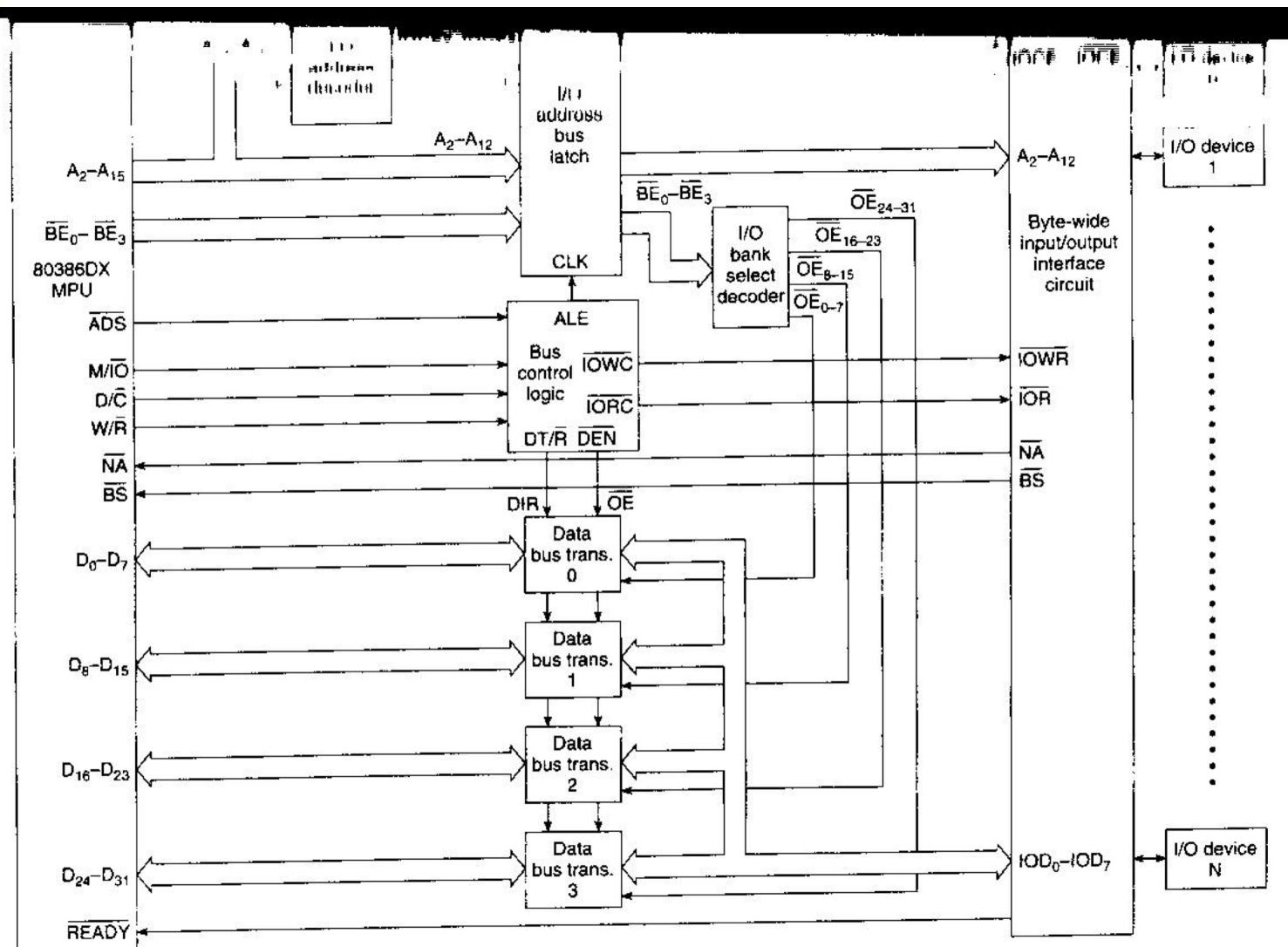


Figure 9.51 Byte-wide I/O interface block diagram.

The 80386, 80486 and Pentium  
Prof. Yan Luo, UMass Lowell