 





Lecture-6 & 7: Blocking and Non-blocking Assignments

ECE-111 Advanced Digital Design Project

Vishal Karna


Winter 2022

Combinational vs Sequential Circuit

 

Combinational Circuit

 - ❑ At any instance of time present value of outputs depends solely on present value of inputs
- ❑ Does not store any intermediate values and hence does not require any memory elements
- ❑ Behavior is described by set of output functions
- ❑ **Examples:** Full Adder, half adder, comparator, multiplexer, decoder, encoder, etc



Sequential Circuit

- ❑ Present values of outputs are determined from present values of inputs and past state (i.e. sequence of past inputs or known as past outputs)
- ❑ Behavior is described by set of output functions and set of next states functions stored in memory
- ❑ It contains memory elements to store past outputs
- ❑ **Examples:** Flipflop, Latch, Shift Register, etc

posedge and negedge event

❑ Positive edge (**posedge**) defines a **rising edge** of a signal


❑ Posedge event triggers when a signal transitions from:

- 0 to 1
- 0 to X
- X to 1
- 0 to Z
- Z to 1

❑ Negative edge (**negedge**) defines a **falling edge** of a signal

❑ Negedge event triggers when a signal transitions from:

 - 1 to 0
- 1 to X
- X to 0
- 1 to Z
- Z to 0



Overview of Always Block

```
always@(<sensitivity list>) begin  
  <procedural statements>  
end
```

```
always@(a or b) begin  
   $c = a \wedge b$ ; // executes if value of 'a' or 'b' changes  
end
```

❑ **always procedural blocks are used to describe events that should happen under certain conditions**

- whenever any event in the sensitivity list occurs, the procedural statements are executed
- sensitivity list can have one or more signals specified
- **always block runs continuously throughout the simulation !**

❑ **Event in sensitivity list can be specified in multiple different ways :**

- Edge (posedge, negedge)
- Level (any change in value of signal)

```
// always block sensitive to  
// posedge event of clock  
always@(posedge clock) begin  
  dout = din;  
end
```

```
// always block sensitive to  
// negedge event of clock  
always@(negedge clock) begin  
  dout = din;  
end
```

```
// always block is sensitive to both  
posedge and negedge event of interrupt  
always@(interrupt) begin  
  abort = 1;  
end
```

Overview of Always Block

❑ Always procedure can be used to model :

- Combinational logic
- Clocked sequential logic (such as flipflops)
- Level sensitive logic (such as latches)

❑ Sequential Logic is triggered by a 'CLOCK' event

- Latches are sensitive to level of the signal
- Flip-flops are sensitive to the transitioning of clock
 - Synthesis compiler will infer a flip-flop if sensitivity list has **posedge** or **negedge** event

```
module flop (  
  input logic clk, d,  
  output logic q);
```

```
  always@(posedge clk)  
  begin  
    q <= d;  
  end  
endmodule
```

Always block triggers
upon rising edge of clk.
posedge CLOCK event
and "<=" will infer
storage and sequential
logic

Sequential Logic using Posedge CLOCK Event

```
module comb (  
  input logic inv, input logic [3:0] data,  
  output logic [3:0] result);
```

```
  always@(inv, data) begin  
    if(inv) result = ~data;  
    else   result = data;  
  end  
endmodule
```

Always block triggers if
either inv or data value
changes. No storage
created. Purely
combinational logic
inferred

Combinational Logic

SystemVerilog Procedural Assignments

- ❑ SystemVerilog has two types of procedural assignments to model combinational and sequential circuits/logic
 - **Blocking Assignments** represented with equal sign (=) to model combinational logic
 - **Non-Blocking Assignments** represented with less-than-equal (<=) to model sequential logic, such as flip flops, latches, shift registers, etc

Blocking Assignment

❑ Blocking Assignment :

- **Syntax :** LHS Variable_Name = [delay or event control] RHS_Expression;
- **Example :**

```
integer a, b, c, sum, prod;
```

```
initial begin
```

```
  a=5; b=10; c=4; sum=2; prod=8;
```

```
  sum = a + b;
```

```
  prod = sum * c;
```

```
end
```

Statements with Blocking assignment will execute one at a time in the order it is specified. Hence **sum = a + b** line will block execution of line **prod = sum * c** until a + b addition is computed and new value of addition is assigned to variable sum

Simulation Result

- Initial values of a=5, b=10, c=4, sum=2, prod=8
- sum becomes (5 + 10) = 15
- prod becomes (15 * 4) = 60

▪ Evaluation and assignment in a single step

- Expression on RHS of (=) assignment is evaluated and the variable on LHS is updated immediately before the next sequential statement in the procedural block is evaluated and executed.
- Execution flow within the procedure is blocked until the current assignment is completed
 - Hence blocking assignment statement is used to model **combinational logic**.
- Each blocking assignment statement executes sequentially in the order it is specified in a procedural block

Non-Blocking Assignment

❑ Non-Blocking assignment :

- **Syntax :** LHS Variable_Name **<=** [delay or event control] RHS_Expression;
- **Example :**

```
integer a, b, c, sum, prod;
```

```
initial begin
```

```
    sum <= a + b;
```

```
    prod <= sum * c;
```

```
end
```

Both statements with non-blocking assignment will execute concurrently without blocking each other

Simulation Result

- At time 0 ns, Initial values a=5, b=10, c=4,
- At time 1 ns,
 - ❖ sum becomes $(5 + 10) = 15$
 - ❖ prod becomes $(2 * 4) = 8$

- **Evaluation and assignment is a two-step process**
 - Expression on RHS of (**<=**) assignment is evaluated immediately
 - Assignment to LHS variable is postponed until other evaluations in **current time step** is completed
 - Latest RHS value is assigned to target LHS variable at the end of the simulation cycle
- Each non-blocking assignment statement within the procedural block executes in parallel (concurrently) without blocking each other
 - Hence the **order of specifying non-blocking assignment statement does not matter !**
- Clock-to-Q propagation delay of flip-flop behavior is represented by non-blocking assignments in RTL model even though RTL code is modeled with zero-delays.
 - Hence non-blocking is used to model **sequential logic**

Blocking vs Non-Blocking Assignment

```
module blocking_assignment (  
    input logic clock, a,  
    output logic b  
);  
always@(posedge clock)  
begin  
    a = 1;  
    // a is '1'  
    b = a;  
    // b is now '1' as well  
end  
endmodule
```

```
module non_blocking_assignment (  
    input logic clock, a,  
    output logic b  
);  
always@(posedge clock)  
begin  
    a <= 1;  
    b <= a;  
    // all assignments are made  
    // b is not yet '1'  
end  
endmodule
```


- ❑ Value is assigned immediately.

- ❑ Process waits until the first assignment is complete, **it blocks progress**


- ❑ Values are assigned at the end of the block.

- ❑ All assignments are made in parallel, **process flow is not-blocked.**

 SystemVerilog RTL Modeling and Verification Events Scheduling Flow



 SystemVerilog RTL Modeling Events Scheduling Flow



Swapping of variables using blocking and non-blocking assignment

```
always@ (posedge clock)
```

```
p = q;
```

```
always@ (posedge clock)
```

```
q = p;
```

Simulation Result

- ❑ Both always blocks will execute concurrently and there is a **race condition** between two always procedural assignments
- ❑ Assume Initial Value of **p=5** and **q=8**
 - If simulator executes always block with **p = q** first, before **q = p**, then both **p** and **q** will get value of **q** (Final values : **p=8** and **q=8**)
 - If simulator executes always block with **q = p** first, before **p = q**, then both **p** and **q** will get value of **p** (Final values : **p=5** and **q=5**)
 - **No Swapping of values of p and q !!**

```
always@ (posedge clock)
```

```
p <= q;
```

```
always@ (posedge clock)
```

```
q <= p;
```

Simulation Result

- ❑ Both always blocks will execute concurrently, however there is no race condition and **actual swapping of values of p and q happens !!**
- ❑ RHS variables are read first and assigned to LHS at the end of the simulation cycle and new RHS variable is available at the next posedge of the clock
- ❑ Assume Initial Value of **p=5** and **q=8**
 - **p** gets previous value of **q**, hence **p=8**
 - **q** get previous value of **p**, hence **q=5**

Swapping of variables using blocking assignment

```
always@(posedge clock) begin
    p = q;
    q = p;
end
```

Simulation Result

- ❑ Simulator executes $p = q$ statement first and then executes $q = p$.
- ❑ Assume Initial Value of $p=5$ and $q=8$
 - Both p and q will get value of q .
There is no swapping of values of p and q !!
 - Final value of $p=8$ and $q=8$

```
always@(posedge clock) begin
    tmp1 = p;
    tmp2 = q;
    p = tmp2;
    q = tmp1;
end
```

Simulation Result

- ❑ **Swapping of values of p and q happens !!**
- ❑ To swap values of p and q using blocking assignment requires temporary variables as shown above
- ❑ Assume Initial value of $p=5$ and $q=8$
 - $tmp1$ will get assigned 5
 - $tmp2$ will get assigned 8
 - p will get assigned value of $tmp2$, which is 8, same as value of q
 - q will get assigned value of $tmp1$, which is 5, same as previous value of p

Sequential Procedural Assignments with Inter-Delay

- ❑ A sequential **blocking assignment** evaluates and assigns before continuing within procedure block
 - Timing control before an assignment statement (**inter assignment delay**) will postpone when the next statement is evaluated and updated
 - **Order of evaluation is deterministic**

```
always@(posedge clk) begin
```

```
  a = 1; —————> Evaluate RHS and assign to 'a' immediately
```

```
  #4 b = a + 2; —————> After execution of previous statement, advance 4 time units due to inter  
end                               assignment delay, then evaluate RHS (a+2) and assign it to 'b' immediately
```

Simulation Output

Assume At **0ns** a=0, b=0

At 1st posedge of clk a=1

At 1st posedge of clk+**4ns** b=3




```
always@(posedge clk) begin
```

```
  a = 1;
```

```
  #4 ns;
```

```
  b = a + 2;
```

```
end
```

 

Note : Event driven simulator will not re-evaluate value of 'a' and 'b' at 34ns and 54ns since there was no change in 'a' or 'b' value

Sequential Procedural Assignments with Inter-Delay

- ❑ A sequential **non-blocking** assignment evaluates, then continues on to the next timing control before next non-blocking assignment evaluates. And then finally updates all LHS variable
 - Timing control before an assignment statement (**inter assignment delay**) will postpone when the next assignment is evaluated and updated
 - **Order of evaluation is deterministic**

```
always@(posedge clk) begin
```

```
  a <= 1; —→ Evaluate RHS immediately; then assign to 'a' at the end of the time step
```

```
  #4 b <= a + 2; —→ Delay 4 time units due to inter assignment delay, then evaluate RHS; then  
end                    assign to 'b' at the end of time step (1 clock period + 4ns)
```

Simulation Output

Assume At 0ns a=0, b=0

At 1st posedge clk, a=1

At 1st posedge clk+4ns, b=3

↕ equivalent


```
always@(posedge clk) begin
```

```
  a <= 1;
```

```
  #4 ns;
```

```
  b <= a + 2;
```

```
end
```

 

Note : Event driven simulator will not re-evaluate value of 'a' and 'b' at 34ns and 54ns since there was no change in 'a' or 'b' value

Concurrent Procedural Assignments with Inter-Delay

- ❑ A concurrent **blocking assignments** have unpredictable results due to race condition
 - **Order of concurrent evaluation is indeterministic and unpredictable simulation result !**

```
always@(posedge clk) begin
```

```
  #4 a = a + 2; —————> Delay 4 time units due to inter assignment delay, then evaluate RHS  
end                                and assign to 'a', immediately
```

```
always@(posedge clk) begin
```


```
  #4 b = a + 3; —————> Delay 4 time units due to inter assignment delay, then evaluate RHS  
end                                and assign to 'b', immediately
```

Simulation Output

Assume At 0ns a=0, b=0

Unpredictable Result !!

 new value of 'b' could be evaluated before or after 'a' changes



Note : Result shown above is in case when simulator evaluates 'b' after 'a' is evaluated

Concurrent Procedural Assignments with Inter-Delay

- ❑ A concurrent **non-blocking assignments** have predictable results
 - **Order of concurrent evaluation is indeterministic, but predictable simulation result !**

```
always@(posedge clk) begin
```

```
  #4 a <= a + 2; ————— Delay 4 time units due to inter assignment delay, then evaluate RHS;  
end                               then assign to 'a' at the end of time step (1 clock period + 4ns)
```

```
always@(posedge clk) begin
```


```
  #4 b <= a + 3; ————— Delay 4 time units due to inter assignment delay, then evaluate RHS;  
end                               then assign to 'b' at the end of time step (1 clock period + 4ns)
```

Simulation Output

Assume At 0ns a=0, b=0

Predictable Result !!

After 1st posedge clk + 4ns
a=2 and b=3

 

Procedural Assignments with Intra-Delays

- ❑ An intra-assignment delay places the timing control after the assignment token
 - Right-hand side is evaluated before the delay
 - Left-hand side is assigned after the delay
- ❑ A sequential **blocking** assignment with intra-delay

```
always@(posedge clk) begin
```

```
  a = 1; —————> Evaluate RHS and assign to 'a' immediately
```

```
  b = #4 a + 2; —————> After execution of previous statement, evaluate RHS expression immediately, then after intra delay of 4 time units assign to 'b'
```

```
  c = #2 b + 2; —————> After execution of previous statement, evaluate RHS expression immediately, then after intra delay of 2 time units assign to 'c'
```

```
end
```


Simulation Output

Assume At 0ns a=0, b=0, c=0

At 1st posedge clk, a=1

At 1st posedge clk+4ns, b=3

At 1st posedge clk+6ns, c=5

 

Procedural Assignments with Intra-Delays

- A sequential **non-blocking** assignment with intra-delay

```
always@(posedge clk) begin
```

```
  a <= 1; —→ Evaluate RHS immediately; then assign to 'a' at the end of the time step
```

```
  b <= #4 a + 2; —→ Evaluate RHS expression immediately, then after intra delay of 4 time units assign to 'b'
```

```
  c <= #2 b + 2; —→ Evaluate RHS expression immediately, then after intra delay of 2 time units assign to 'c'
```

```
end
```


Simulation Output

Assume At **0ns** a=0, b=0

At 1st posedge clk, a=1

At 1st posedge clk+2ns, c=2

At 1st posedge clk+4ns, b=2

 

Rules

- ❑ It is not recommended to have both blocking and non-blocking assignment statements in same always block.

```
always@(a,b) begin
```

```
    sum = a + b;
```

```
    prod <= a * b;
```

```
end
```



- ❑ Synthesis compiler will ignore inter and intra delays in both blocking and non-blocking procedural assignment statement

- If delays are used, then expect mis-match between RTL and synthesized netlist simulation result

```
always@(a,b) begin
```

```
    c = #2 (a + b); // #2 delay ignored by synthesizer, however in RTL simulation effect of #2 will be observed
```

```
end
```

- ❑ Same variable cannot have both blocking and non-blocking assignments to it. Below mentioned is not allowed !!

```
always@(a,b) begin
```

```
    c <= a + b;
```

```
    c <= a * b;
```

```
end
```



D-FlipFlop Model Using Non-blocking assignment


```
module dff(  
  input logic clk, d,  
  output logic q  
);
```

```
always@(posedge clk) begin
```


```
  q <= d; // when clk rises copy 'd' to 'q'  
end
```

```
endmodule: dff
```

 - SystemVerilog calls “<=“ a “non-blocking” assignment.
- It means “wait until end of current simulation cycle before updating “q”.
- When clk is not rising, value of q is preserved (memorized)
- Synthesis will produce a positive edge-triggered D-FF



 Input 'd' = 1 captured at CLK edge '2' will appear at output 'q' and value of 'q' = 1 will then be preserved until CLK edge '3'




Value of 'q' is retained until next edge of clk

Example of blocking vs non-blocking assignment

```
module parallel_registers (  
  input logic clk, d, // clk is a clock  
  output logic q1, q2  
);  
always @(posedge clk)  
begin  
  q1 = d;  
  q2 = q1;  
end  
endmodule
```

 q1 is not connected to q2
and both q1 and q2 will get
same value of d in same
clock cycle


Synthesis compiler will create two registers in parallel



```
module shift_register (  
  input logic clk, d, // clk is a clock  
  output logic q1, q2  
);  
always @(posedge clk)  
begin  
  q1 <= d;  
  q2 <= q1;  
end  
endmodule
```

 q1 is serially connected to
q2. New value of d is first
propagated to q1 and one
clock cycle later it will
propagate to q2

Synthesis compiler will create two serially chained registers and circuit will behave as a two bit shift register



Note : Serially chained register is known as shift register

Splitting Blocking Assignments in Separate Always Block


```
module shift_register (  
  input logic clk, d,  
  output logic q1, q2  
);
```

```
always@(posedge clk)  
begin  
  q1 = d;  
end
```

```
always@(posedge clk)  
begin  
  q2 = q1;  
end
```

```
endmodule
```

 Splitting blocking assignment statements in two separate always block will result in a two-bit shift register upon synthesis since both assignments will execute in parallel



Synthesis compiler will connect q1 to q2 and circuit will behave as a two-bit shift register

Note : However in simulation due to race condition between two always procedural block based on which always block executes first it might behave as a 2-bit shift register or 1-bit parallel registers.



- If always block with q2=q1 assignment executes first over other always block having q1=d then circuit will behave as a 2-bit shift register
- If always block with q1=d assignment executes first over other always block having q2=q1 then circuit will behave as 1-bit parallel register

Shift Register using Non-Blocking Assignments

```
module shift_register (  
  input logic clk, d,  
  output logic q  
);  
  logic[2:0] t;  
  always@(posedge clk)  
  begin  
    t[0] <= d;  
    t[1] <= t[0];  
    t[2] <= t[1];  
    q <= t[2];  
  end  
endmodule
```

Since all RHS
expression will be
evaluated in
parallel, non-
blocking
assignments can be
specified in any
order

Simulation Result

 
 


Shift Register using Blocking Assignments (Incorrect Usage)

```
module incorrect_shift_register (  
  input logic clk, d,  
  output logic q  
);  
  logic[2:0] t;  
  always@(posedge clk)  
  begin  
    t[0] = d;  
    t[1] = t[0];  
    t[2] = t[1];  
    q = t[2];  
  end  
endmodule
```

Due to blocking assignment, this code can be seen as $d=q$ and this will behave as a 1-bit register.

Simulation Result

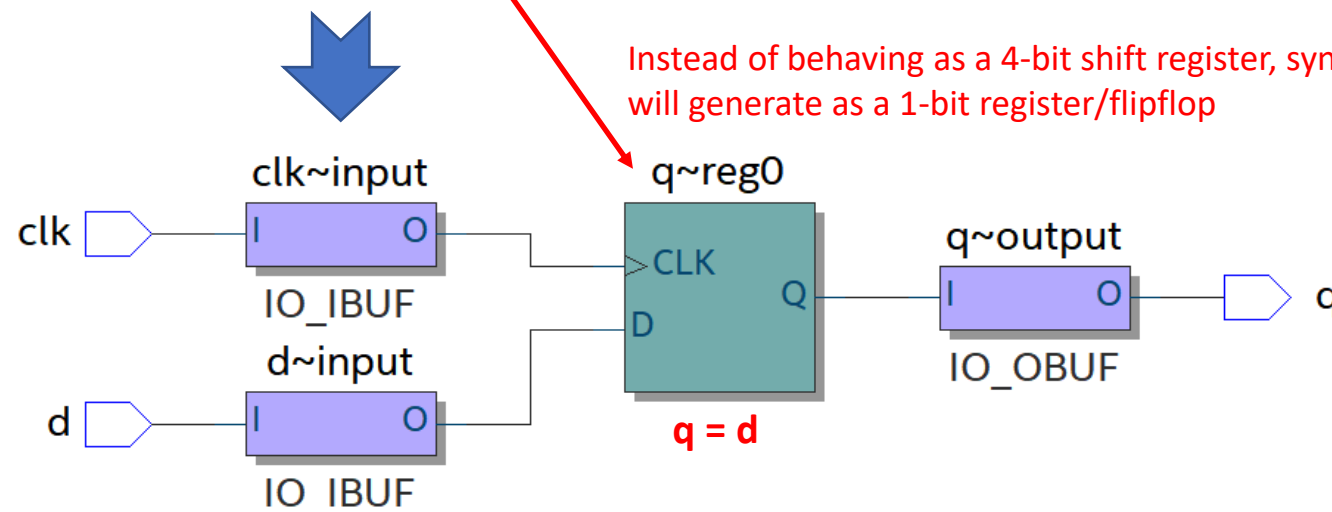 

Shift Register using Re-ordered Blocking Assignments



```

module shift_register (
    input logic clk, d,
    output logic q
);
    logic[2:0] t;
    always@(posedge clk)
    begin
        q = t[2];
        t[2] = t[1];
        t[1] = t[0];
        t[0] = d;
    end
endmodule

```

Ordering of blocking assignment is important.
Re-ordering blocking assignment statements can result in a different circuit, in this case it became a shift register

Simulation Result

  

References

- ❑ **SystemVerilog Event Regions, Race Avoidance & Guidelines** : SNUG Conference 2006
 - **Paper Authors** : Clifford E. Cummings (Sunburst Design), Arturo Salz (Synopsys)
 - http://www.sunburst-design.com/papers/CummingsSNUG2006Boston_SystemVerilog_Events.pdf