 


Lecture 5: Reversible (Deterministic) Computation

Inverse = Reverse:


• "Hat" $\rightarrow$ Hadamard (H)

• Deterministic :



"Add A to B"

sample circuit diagram

 


"Add $F(x_1, x_2, x_3, \dots)$ To Answer"
examples

<u>F</u>	<u>Instruction</u>	<u>Real name</u>	<u>Diagram</u>
$F() = 0$	Add 0 to Ans (does nothing)	I	()
$F() = 1$	Add 1 to Ans	NOT, X	NOT, $\oplus$
$F(x_1) = x_1$	Add x_1 to Ans	Controlled - NOT, or CNOT	
$F(x_1) = \neg x_1$	Add (NOT x_1) to Ans	C ₀ NOT	
$F(x_1, x_2) = x_1 \text{ AND } x_2$	Add ($x_1 \text{ AND } x_2$) to Ans	Controlled - CNOT, CCNOT, Toffoli	
$F(x_1, x_2) = x_1 \text{ OR } x_2$	Add ($x_1 \text{ OR } x_2$) to Ans		

Other reversible det. instructions:

LeftShift (A, B, C) $^{-1}$ = RightShift (A, B, C)

L/R Shift (A, B) $\equiv$ SWAP (A, B)

 

"Compute - A - Function Tasks":

$F: \{0,1\}^n \rightarrow \{0,1\}^m$
input output

$n=3, m=2$

e.g.: Count: $\{0,1\}^3 \rightarrow \{0,1\}^2$

Count (x_1, x_2, x_3) = $y = (y_1, y_2)$

	input			output		
Truth Table of Count	0	0	0	0	0	0
	0	0	1	0	1	0
	0	1	0	0	1	0
	0	1	1	1	0	0
	1	0	0	0	1	0
	1	0	1	1	0	0
	1	1	0	1	0	0
	1	1	1	1	1	1

MAY ↑ XOR

$$\text{Count}(x_1, x_2, x_3) = y = (y_1, y_2)$$

binary rep. of # 1's in input

Q0: Can every truth table be computed by an AND/OR/NOT circuit?

Q1: How efficiently?

A0: Yes.

Obs.: can assume # output bits is $m=1$.

Obs.: Suffices to solve functions of the form

"Is Input 110?" : $\{0,1\}^3 \rightarrow \{0,1\}$


$$\text{MAT}(x_1, x_2, x_3) = ((\text{Is } 011?(x) \text{ OR } \text{Is } 101?(x))$$

$$\text{OR } \text{Is } 110?(x))$$

$$\text{OR } \text{Is } 111?(x))$$

in	out
000	0
001	0
...	...
110	1
111	0

Is 110? (x_1, x_2, x_3) :

 

reversible form

Given x_1, x_2, x_3 :

$$g1 := \text{NOT } x_3$$

$$g2 := x_1 \text{ AND } x_2$$

$$g3 := g1 \text{ AND } g2$$

$$\text{answer} := g3$$

$:= \rightarrow$
add R to
ANS

Given x_1, x_2, x_3

Initialize $g1, g2, g3$, ans to 0

Add NOT x_3 to $g1$

Add $x_1 \text{ AND } x_2$ to $g2$

Add $g1 \text{ AND } g2$ to $g3$


Add $g3$ to ans

"Trashy - Add Is110? (x_1, x_2, x_3) To Ans":

// precondition: assumes temp vars g_1, g_2, g_3 set to 0

Add (NOT x_2) to g_1	}	$C_0 \text{NOT} (x_2, g_1)$
Add ($x_1 \text{ AND } x_2$) to g_2		$CC \text{NOT} (x_1, x_2, g_2)$
Add ($g_1 \text{ AND } g_2$) to g_3		$CC \text{NOT} (g_1, g_2, g_3)$
Add g_3 to Ans		$C \text{NOT} (g_3, \text{Ans})$

 // postcondition: g_1, g_2, g_3 are some trash



Summary: For every $F: \{0,1\}^n \rightarrow \{0,1\}^m$

If you can compute it with a classical
AND/OR/NOT circuit using G gates
then you can convert to reversible
Add - F - to - Ans code

using:

- $n + m + G$ bits in total
- $\approx G$ total instructions
- assumes the extra G vars are initialized to 0, left in a trash state

Moreover: $G \leq n \cdot m \cdot 2^n$ always
 $\leq m \cdot 2^n / n$ [C. Shannon]

Remark: What about using computer code, not circuits?

Theorem: If authn/C/TM code computes a

Remark: ... using ... circuits:

Theorem: If python/C/TM code computes a function $F: \{0,1\}^n \rightarrow \{0,1\}^m$ in T "steps", it can be compiled into AND/OR/NOT circuits with $G \leq \tilde{O}(T^2)$. ✓
(usually $\leq \tilde{O}(T)$)

Taking Out The Trash

Reason 1: Waste of space!

Would be great to restore trash bits to 00...0 by the end.

(Could reuse these temp vars several times.)

Reason 2: "Magic" in q. computing is: amplitudes can cancel out to 0.

0. Make A

1. Had A $\rightarrow$ q. state is now

$$\text{Ampl}[0] = \sqrt{1/2}, \text{Ampl}[1] = \sqrt{1/2}$$

2. Had A $\rightarrow$ $\text{Ampl}[0] = 1$ $\text{Ampl}[1] = \frac{1}{2} - \frac{1}{2} = 0$

3. Print A
100% chance
 $A=0$!

$\rightarrow$ say replaced by many instructions

but say they create $q_1, \dots, q_4$ are all 0

Then after line 1: $\text{Ampl}(\underset{\substack{\uparrow \\ q_1, \dots, q_4}}{0}, 0000) = \sqrt{1/2}$

$$\text{Ampl}(1, 0000) = \sqrt{1/2}$$

After line 2:

$$\text{Ampl}(0, 0000) = 1$$

$$\text{Ampl}(1, 0000) = 0$$

$$\text{Ampl}(0, 0000) = 1$$

$$\text{Ampl}(1, 0000) = 0$$


Print All $\rightarrow$ 100% $A=0$ (& q 's are 0)

$\rightarrow$ OTOM, say line 1 replaced by instrs that leave $q_1, \dots, q_4$ in some trashy units

eg: $\text{Ampl}(0, 0111) = \sqrt{1/2}$

$\text{Ampl}(1, 1100) = \sqrt{1/2}$

Now if we do Line 2: Had A

 

Final: $\text{Ampl}(00111) = 1/2$

$\text{Ampl}(10111) = 1/2$

$\text{Ampl}(01100) = 1/2$

$\text{Ampl}(11100) = -1/2$

$\rightarrow$ Print All

$\Rightarrow \frac{1}{2}$ prob. $A=0$

$\frac{1}{2}$ prob. $A=1$

garbage-free $\rightarrow$ ~~Trashy~~ "Add Is110?(x_1, x_2, x_3) to Ans":
// precondition: g_1, g_2, g_3 initialized to 0

Reverse! $\left\{ \begin{array}{l} \text{Add (NOT } x_3) \text{ to } g_1 \\ \text{Add } (x_1 \text{ AND } x_2) \text{ to } g_2 \\ \text{Add } (g_1 \text{ AND } g_2) \text{ to } g_3 \\ \text{Add } g_3 \text{ to Ans} \end{array} \right.$
// Ans is good, but g_1, g_2, g_3 are trash

$\left\{ \begin{array}{l} \text{Add } (g_1 \text{ AND } g_2) \text{ to } g_3 \\ \text{Add } (x_1 \text{ AND } x_2) \text{ to } g_2 \\ \text{Add (NOT } x_3) \text{ to } g_1 \end{array} \right.$

// postcondition: g_1, g_2, g_3 restored to 0

We can always make deterministic reversible code garbage-free with $\leq 2 \cdot G$ instructions